



DANISH
HANIF
HELP BY DANISH



Paid Services Available 10/10 Marks Guarantee

WhatsApp Contact: 0323-1731413

CS302 Quiz File

6/7/2023 9:54:05 PM

1) The simplified expressions using either of the two K-maps are _____.

Select the correct option

- A. Similar
- B. **Identical**
- C. Different
- D. Non-identical

2) The _____ select input(s) of the two 4-input multiplexers are common in Dual 4-input multiplexer.

Select the correct option

- A. **Two**
- B. Four
- C. Three
- D. One

3) The look-ahead carry circuits _____

Select the correct option

- A. Determine sign and magnitude
- B. Add a 1 to complemented inputs
- C. Increase ripple delay
- D. **Reduce propagation delay**

4) Adjacent 1s detector circuit will have active high output for the input

Select the correct option

- A. 0101
- B. 1010
- C. **0011**

D. 0001

5) The Decimal-to-BCD Encoder has _____ outputs

Select the correct option

A. 10

B. 4

C. 2

D. 16

6) The GAL22V10 is a popular GAL device having _____ inputs and ten inputs/outputs.

Select the correct option

A. 22

B. 10

C. 20

D. 12

7) In 16-bit ALU, the Carry Out 16 is generated only when ALU3 has received Carry In ____.

Select the correct option

A. 4

B. 8

C. 12

D. 2

8) Multiplexers are also known as _____.

Select the correct option


A. Data Distributors

B. Data Setter

C. Data Selectors

D. Data Manipulators

WHATSAAPP CONTACT 03231731413

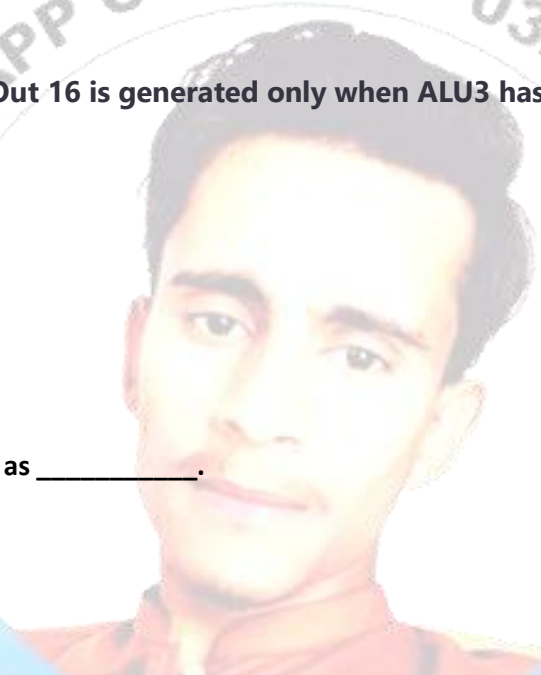

HELP BY DANISH