

11:58 PM



VoWiFi

4G



33.0 K/S



vulms.vu.edu.pk/



Question # 1 of 10 (**Start time: 11:58:05 PM, 03 July 2024**)

Which of the following is correct option about information hiding in software development.

Select the correct option



Validity of module may not be compromised



It only depends on internal compositional structure of modules



It prevents unnecessary dependency between modules



It hides all data of program module

Click to Save

11:33 PM



Vo
WiFi

E



22.5
K/S

35



vulms.vu.edu.pk/



4



(Graded))

Question # 10 of 10 (Start time: 11:32:38 PM, 03 July 2024)

Which of the following gates is used for parity generation for a binary data string?

Select the correct option


☐	AND
☒	XOR
☐	NOR
☐	OR

Click to See

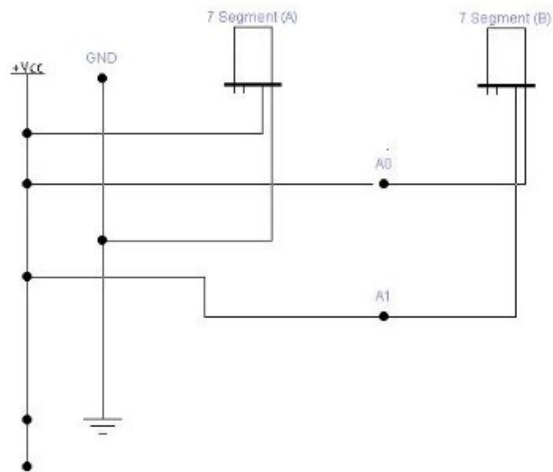Question # 8 of 10 (Start time: 11:30:30 PM, 03 July 2024)

Total Marks: 1

Consider the below given EWB circuit, what values will be displayed on 7-segment displays A and B when the circuit simulation is activated in EWB?



Select the correct option

[Reload Math Equations](#)

☐	2, 3
☐	0, 1
☐	3, 3
☒	1, 3



Click to Save Answer & Move to Next Question



vulms.vu.edu.pk/



4

**CS302P - Digital Logic Design (Practical) (Semester Quiz # 04 (Graded))****Question # 9 of 10 (Start time: 11:32:02 PM, 03 July 2024)**

Convert the Gray code 1011 to binary.

Select the correct option

☐	0111
☐	1010
☒	1101
☐	1011

CS302P - Digital Logic Design (Practical) (Semester Quiz # 04 (Graded))

Question # 7 of 10 (Start time: 11:29:50 PM, 03 July 2024)

To build a full adder using gates, how many gates are required?

Select the correct option

☐	2 AND gates, 2 XOR gates, 1 OR gate
☒	2 AND gates, 2 OR gates, 2 XOR gates
☐	2 AND gates, 3 OR gates, 1 XOR gates
☐	1 AND gate, 2 OR gates, 1 XOR gate

11:27 PM



VoWiFi

4G

28.6 K/S

36



vulms.vu.edu.pk/



4



CS302P - Digital Logic Design (Practical) (Semester Quiz # 04 (Graded))

Question # 5 of 10 (**Start time: 11:27:12 PM, 03 July 2024**)

Don't care conditions can be used for simplifying Boolean expressions in _____.

Select the correct option

☒	K-maps
☐	Registers
☐	Terms
☐	Latches