

CS302P SEMESTER

Quiz 2 2023

BY TEAM Aiza VU

Paid Services Available:

- ***LMS Handling***
- ***Quiz***
- ***Assignments***
- ***GDB***
- ***Lecture View***

Contact US:

TEAM Aiza VU

0320 8459347

1: Which of the following symbols is used to represent XOR operation? Select the correct option



X

+

^

2: The K-map based Boolean reduction is based on the following Unifying Theorem: $A + A' = 1$. Select the correct option

Impact

Force

Complementarity

Non Impact

3: When implementing a half adder by using gates, which of the following gates is used to give Sum (S) as an output? Select the correct option

OR

XOR

AND

NOR

4: In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the multiplexer? Select the correct option

G'

Vcc

Y

M

5: Which of the following is not a valid number for grouping of terms in K-Map?Select the correct option

1

3

4

2

6: Each product term of a group, $w'xy'$ and wy , represents the _____ in that group.Select the correct option

POS

Input

Sum of Maxterms

Sum of Minterms

7: To build a full adder using gates, how many gates are required?Select the correct option

1 AND gate, 2 OR gates, 1 XOR gate

2 AND gates, 2 XOR gates, 1 OR gate

2 AND gates, 2 OR gates, 2 XOR gates

2 AND gates, 3 OR gates, 1 XOR gates

8: Each group of adjacent Minterms (group size in powers of twos) corresponds to a possible product term of the given _____.Select the correct option

Value

Word

Set

Function

9: There are _____ cells in a 4-variable K-map.Select the correct option

20

16

8

24

10: How many select lines would be required for an 8x1 multiplexer?Select the correct option

2

3

1

8

THANK YOU