

PHY301 Assignment#2 Solution 2023


by Artist H 25

~**~☆~**~ Artist H25 ~**~☆~**~


WORD FILE LINK BELOW

C

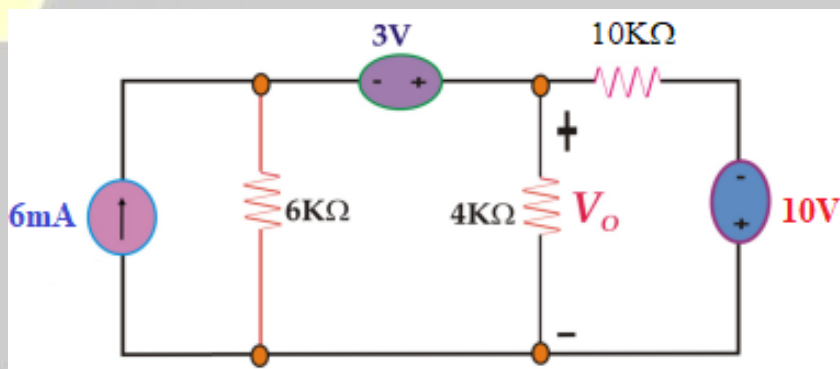
Calculate V_o by source transformation & Loop method. Draw and label the circuit diagram of each step, also mention the unit of each derived value. [Marks:10]




Solution:

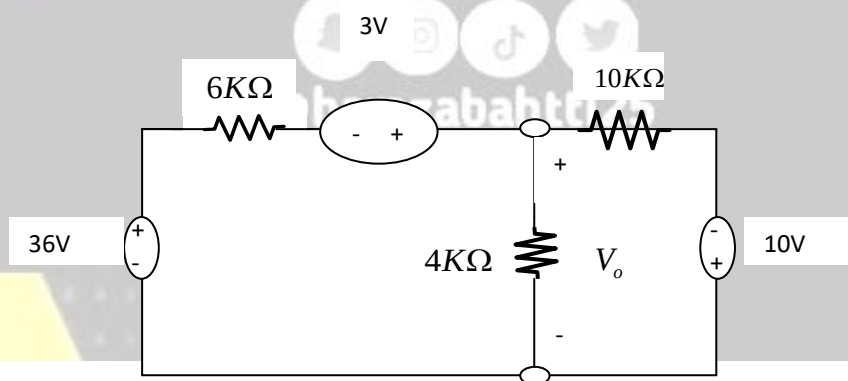


$V=IR$ imply that $v=6 \times 6=36V$

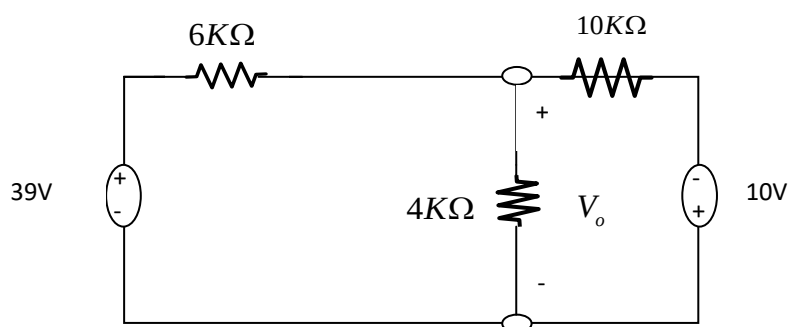

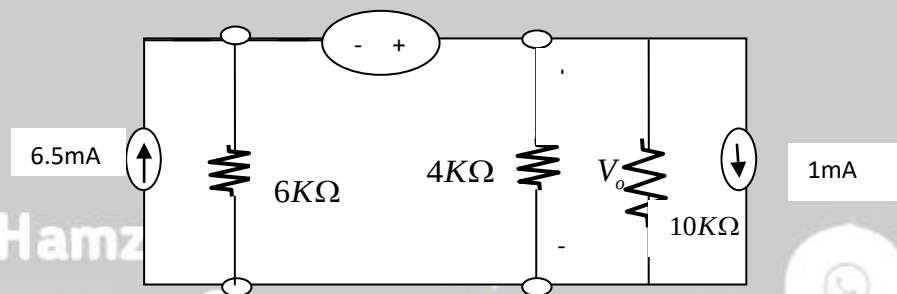$I = V / t = 39/6 = 6.5\text{mA}$ and $10/10 = 1\text{mA}$



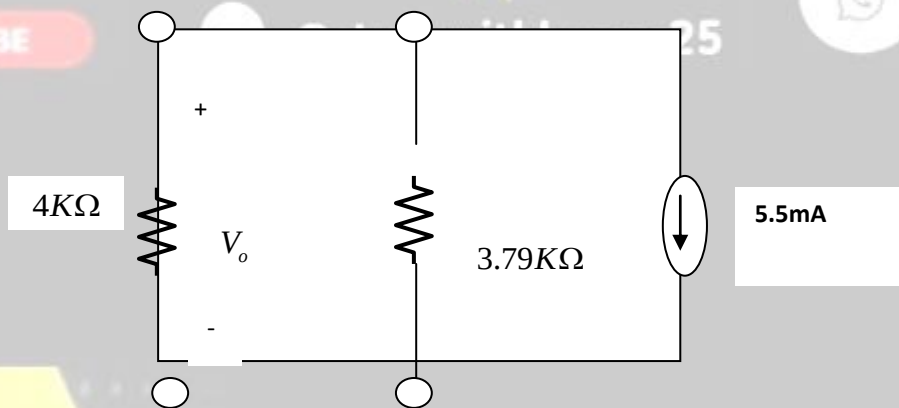$R_t = R_1 \times R_2 / R_1 + R_2 = 6 \times 10 / 6 + 10 = 3.75$



Apply current division Rule:


$$I_{4K\Omega} = 5.5mA \times \frac{3.75}{3.75 + 4} K\Omega = 2.66mA$$

$$V_o = 2.66 \times 4$$

$$= 10.64v$$

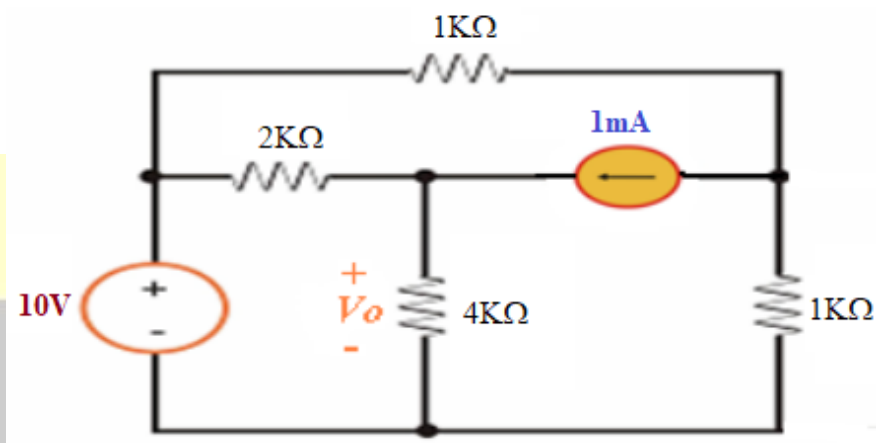Q.2:

Use Thevenin's theorem to find V_o in the network given below.
(Write each step of the calculation & draw circuit diagram where required to get maximum marks)



10KΩ



Study With Hamza

SUBSCRIBE



@studywithhamza25




@hamzabahtti25



03147094561
03217769365

Solution:

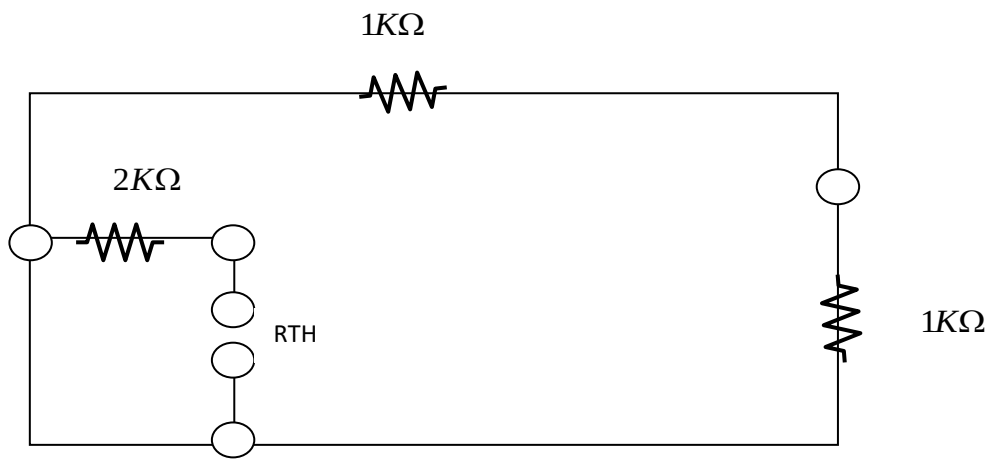

$$R_{TH} = 2K\Omega$$

Because in terminal a and b circuit is open in series resistance will be =0



Study With Hamza

SUBSCRIBE



@studywithhamza25



@hamzabahtti25



03147094561
03217769365

To Find VTH:


Study With Hamza

SUBSCRIBE




 @studywithhamza25


@hamzabahtti25



03147094561
03217769365

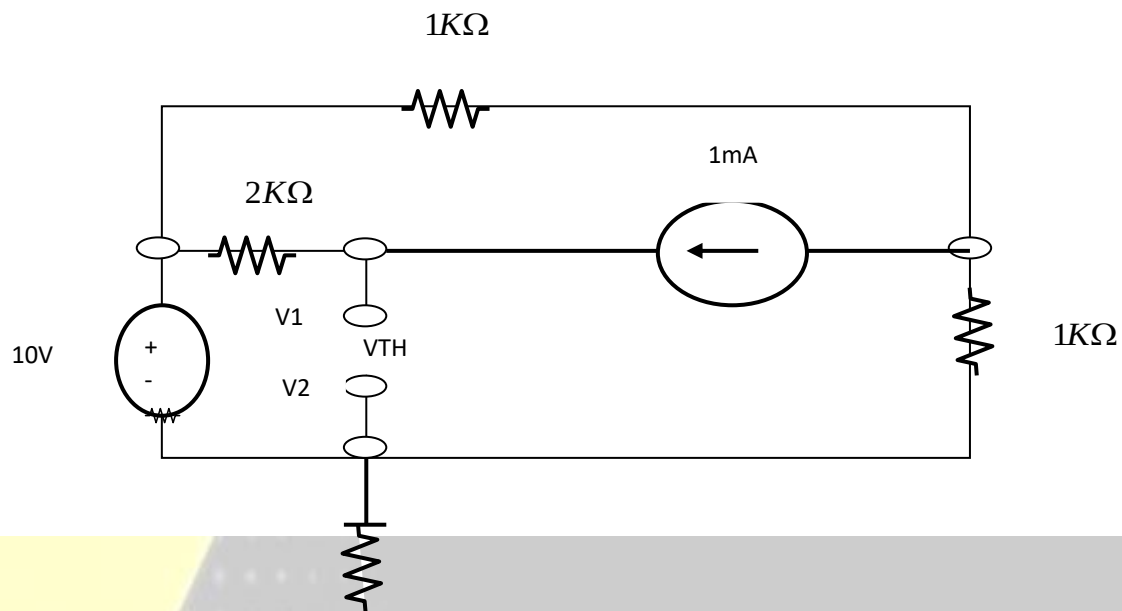

KVL to super mesh

$$-10 \times 10^3 \times I_1 + 1 \times 10^3 \times I_2 = 0$$

$$10^3 \times I_1 - 10^3 \times I_2 = 10$$

Equation 1:

$$10^3 \times I_1 - 10^3 \times I_2 = 10$$

From Super Mesh:

$$I_1 - I_2 = 1 \times 10^{-3}$$

Equation 2:

$$I_1 - I_2 = 1 \times 10^{-3}$$

Solving Equation 1 & 2

$$I_1 = 5.5mA$$

$$I_2 = 4.5mA$$

Apply KVL to MESH 3


$$-10 + 2 \times 10^3(I_2 - I_1) + V_{oc} = 0$$

$$V_{oc} = 10 + 2 \times 10^3(4.5 \times 10^{-3} - 5.5 \times 10^{-3})$$

$$V_{oc} = 12V$$

$$V_{TH} = 12V$$

Thevenin's theorem to find V_o

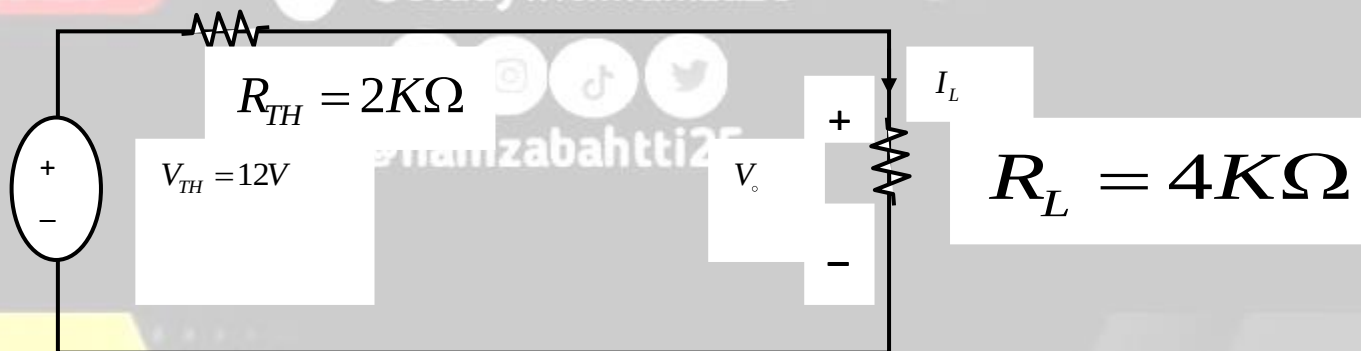

Thevenin's theorem Circuit

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}$$

$$= \frac{12}{2 \times 10^3 + 4 \times 10^3}$$

$$I_L = 2 \times 10^{-3} \text{ mA}$$

$$V_o = I_L \times R_L$$

$$= 2 \times 10^3 \times 4 \times 10^3$$

$$V_o = 8V$$

[WORD FILE](#)



[SUBSCRIBE OUR YOUTUBE CHANNEL](#)



[JOIN WHATSAPP GROUP](#)



Study With Hamza

SUBSCRIBE



@studywithhamza25



@hamzabahtti25



03147094561
03217769365