

# VIRTUAL UNIVERSITY OF PAKISTAN

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI  
EMAIL: [hadirajputofficial@gmail.com](mailto:hadirajputofficial@gmail.com)  
WHATSAPP & CALL: 03087122922

## (Final Term Past Paper)

MADE AND SOLVED BY TEAM HADI

WARNING: Team HADI is not responsible for any mistake or wrong answer. All students reading and using this document may check and confirm the answers at their own.



WhatsApp: 03087122922



FACEBOOK ID: <https://www.facebook.com/hadipastpapers/>

Best of luck!



Which of the following is not correct statement.

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**Answer ( Please select your correct option )**

☐

Proton is 1840 times heavier than electron.

☐

The total number of electrons in the outer rings must equal to the number of protons in the nucleus in a neutral atom.

☐

The electrons in an atom are bound to the protons in the nucleus by the electromagnetic force.

☐

As a whole an atom is not neutral particle.

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

How many electron charges are there in the practical unit of one coulomb.

Answer ( Please select your correct option )

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

☐ 4.5x10<sup>6</sup>

☐ 6.5x10<sup>16</sup>

☒ 6.25x10<sup>18</sup>

☐ 1.9x10<sup>-19</sup>



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

If magnitude of the current is controlled by input current the source is called

Answer ( Please select your correct option )

☐ Current controlled current source

☐ Current controlled voltage source

☐ Voltage controlled voltage source

☐ Voltage controlled current source

**CORRECT ANSWER SOLVED BY IIADI**

**CELL NO: 03228043306**

**EMAIL: IIADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Current divider is used when

**CORRECT ANSWER SOLVED BY TIADI**  
**CELL NO: 03228043306**  
**EMAIL: TIADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please select your correct option )

- ☐ Two or more resistances are in series of a voltage source
- ☐ Two or more resistances are in parallel of a voltage source
- ☐ Two or more resistances are in series of a current source
- ☐ Two or more resistances are in parallel of a current source

correct

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMA**

Leakage current of semiconductor diode is caused by

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please select your correct option )

☐ chemical energy

☐ heat energy

☐ barrier voltage

☐ doping impurity

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Distance or link between two nodes is called

Answer ( Please select your correct option )

- ☐ Branch
- ☐ Loop
- ☐ node
- ☐ super mesh



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

Using superposition theorem, for a circuit containing independent sources, any remaining current source is

Answer ( Please select your correct option )

- ☐ replaced by short circuit
- ☐ made zero by replacing them by open circuit
- ☐ replaced by close circuit
- ☐ replaced by capacitor

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**


correct

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

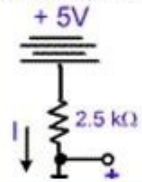**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Considering diode to be ideal , current flowing through resistance will be



Answer ( Please select your correct option )

☐ 5mA

☐ 2mA

☐ zero ampere

☐ 2.5mA

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**


**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**


**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

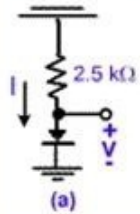

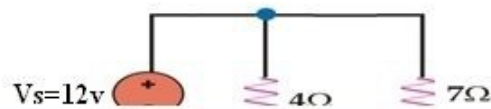**CORRECT ANSWER SOLVED BY IIADI****CELL NO: 03228043306****EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM****Answer ( Please select your correct option )**☐ 5mA☐ 2mA☐ zero ampere☐ 2.5mA**CORRECT ANSWER SOLVED BY HADI****CELL NO: 03228043306****EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Across which resistance more voltage is dropped



Answer ( Please select your correct option )

- ☐ 4Ω
- ☐ 7Ω
- ☐ same across both
- ☐ no voltage drop

**CORRECT ANSWER SOLVED BY HADI**


**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

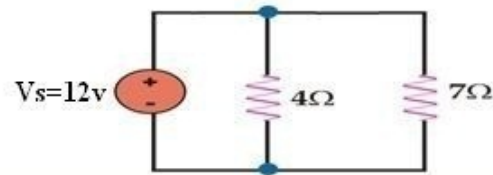

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

Answer ( Please select your correct option )

- ☐ 4Ω
- ☐ 7Ω
- ☐ same across both
- ☐ no voltage drop



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

Through which resistance least current will flow



Answer ( Please select your correct option )

☐ 50Ω


☐ 30Ω

☐ 20Ω

☐ same through all resistance

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

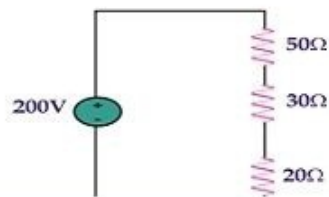**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**




Answer ( Please select your correct option )

- ☐ 50Ω
- ☐ 30Ω
- ☐ 20Ω
- ☐ same through all resistance

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

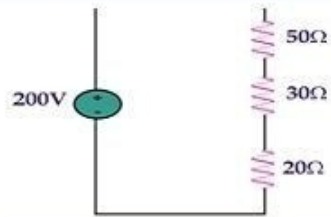**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**





Answer ( Please select your correct option )

**CORRECT ANSWER SOLVED BY TIADI**  
**CELL NO: 03228043306**  
**EMAIL: TIADIRAJPUTOFFICIAL@GMAIL.COM**

☐ 50Ω

☐ 30Ω

☐ 20Ω

☐ same through all resistance

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Which of the following statement is not correct?


Answer ( Please select your correct option )

- ☐ An open circuit has zero current.
- ☐ A short circuit has excessive current.
- ☐ An open circuit and a short circuit have opposite effects on resistance and current.
- ☐ A closed circuit do not allow flow of current

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**

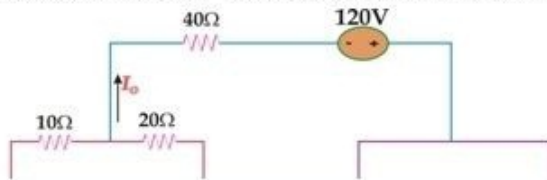How many sources are dependent sources in given circuit?



Answer ( Please select your correct option )

☐ 3


☐ 2

☐ 4

☐ 1

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

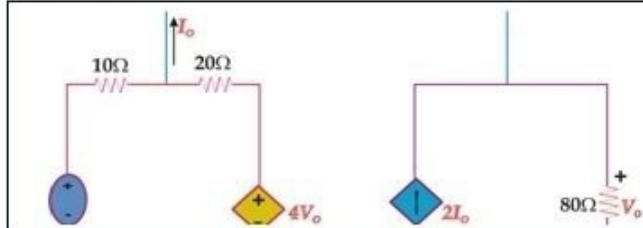**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Answer ( Please select your correct option )

3

☐

2

☐

4

☐

1

☐

CORRECT ANSWER SOLVED BY HADI


CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

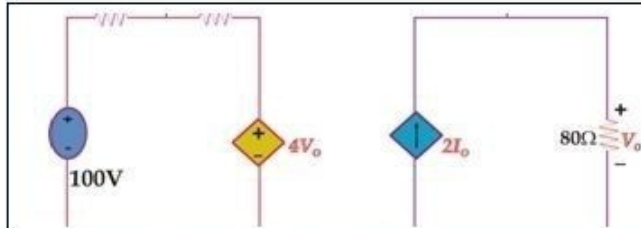

Answer ( Please select your correct option )

☐ 3☐ 2☐ 4☐ 1**CORRECT ANSWER SOLVED BY HADI****CELL NO: 03228043306****EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM****CORRECT ANSWER SOLVED BY HADI****CELL NO: 03228043306****EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Question No : 12 of 43

Marks: 1 (Budgeted Time 1 Min)



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

Answer ( Please select your correct option )

3


2

4

1

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

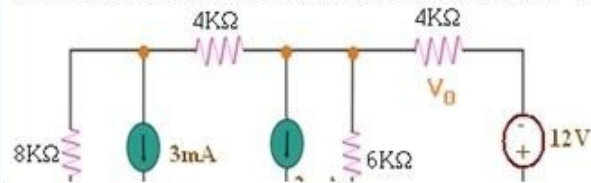Converting 12v voltage source into current source, value of converted current source will be



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please select your correct option )


☐ 3mA

☐ 2mA

☐ 48mA

☐ 1mA

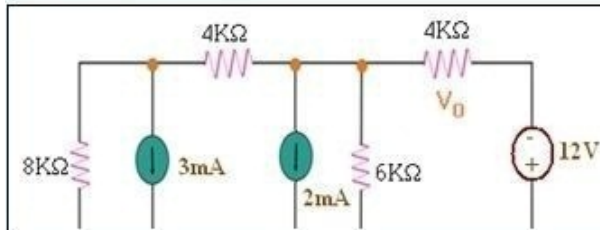**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**




Answer ( Please select your correct option )

☐ 3mA☐ 2mA☐ 48mA☐ 1mA

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

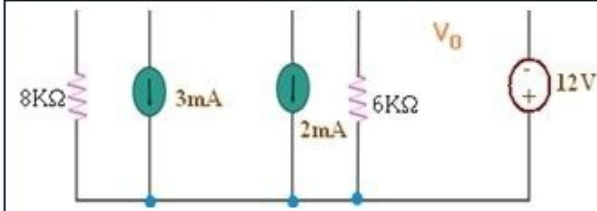**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Answer ( Please select your correct option )

- ☐ 3mA
- ☐ 2mA
- ☐ 48mA
- ☐ 1mA

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

In a Norton's theorem ,norton's current **Inor** is calculated

Answer ( Please select your correct option )

- ☐ at open terminals of the open circuit
- ☐ by short circuiting the open terminal of the circuit
- ☐ across the load
- ☐ any where

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Semiconductor element in pure form is called

Answer ( Please select your correct option )

☐ extrinsic

☐ P type

☒ intrinsic

☐ N type



CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

A transformer is used for

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please select your correct option )

☐ dc voltage

☐ ac voltage

☐ both ac and dc voltage

☐ none of these

i think

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

For secondary turns of 10 and primary turns of 20, turn ratio is

Answer ( Please select your correct option )

☐ 20:20

☐ 10:20

☐ 10:10

☐ 20:10

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

The depletion region of a semiconductor diode is due to

Answer ( Please select your correct option )

☐ Absence of current carriers

☐ Reverse biasing

☐ Forward biasing

☐ Crystal doping

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

The PIV of a half wave rectifier is

Answer ( Please select your correct option )

☐  $V_{(pk)}$

☐  $2V_m$

☐  $V_m/2$

☐  $3V_m$

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



The leakage current of semiconductor diode is caused by

Answer ( Please select your correct option )

☐ Chemical energy

☐ Barrier voltage

☐ Heat energy

☐ Doping impurity

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

As diode conducts the electrical current only in one direction, hence it is consider as a

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please select your correct option )

☐ Switch

☐ Amplifier

☐ Capacitor

☐ Inductor

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

The base region of a p-n-p transistor is

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please select your correct option )

- ☐ Very thin and heavily doped with holes
- ☐ Very thin and heavily doped with electrons
- ☐ Very thin and lightly doped with holes
- ☐ Very thin and lightly doped with electrons

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

In normal /active operation, the junctions of a p-n-p transistor are:

Answer ( Please select your correct option )

- ☐ Both forward biased
- ☐ Base-emitter forward biased and base collector reverse biased
- ☐ Both reverse biased
- ☐ Base-collector forward biased and base-emitter reverse biased

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

For a transistor, if value of  $\alpha$  is 0.9, and the emitter current( $I_E$ ) is 4mA, then

Answer ( Please select your correct option )

- ☐ The base current is approximately 4.4mA
- ☐ The collector current ( $I_C$ ) is approximately 3.6mA
- ☐ The collector current is approximately 4.4mA
- ☐ The base current is approximately 3.6mA

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



What will happen when  
(I) two like charges come close  
(II) two opposite charges come close

Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Mention the P- type and n- type for Diode symbol given below.



Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**


**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

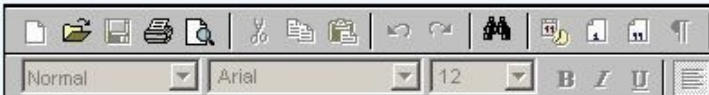**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Write the formula to calculate PIV for half wave rectifier.

Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

What is the relationship between the polarity of the voltage applied to the PNP transistor and that applied to the NPN transistor?


**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

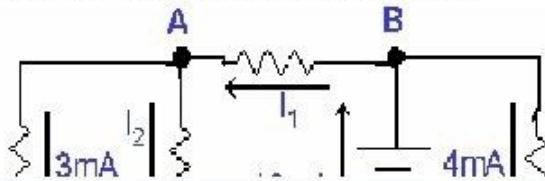Write KCL equation for node A and node B.




Answer ( Please [click here](#) to Add Answer )

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

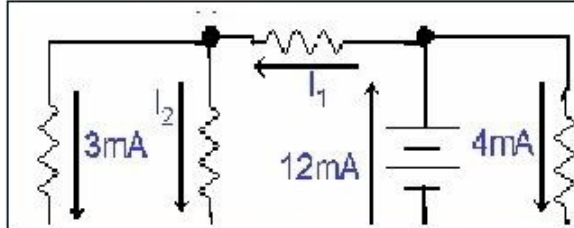CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM





Answer ( Please [click here](#) to Add Answer )



CORRECT ANSWER SOLVED BY HADI


CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

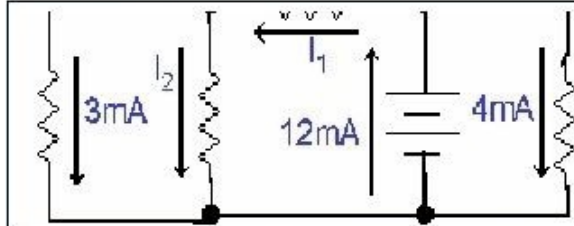

Answer ( Please [click here](#) to Add Answer )



CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306


EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

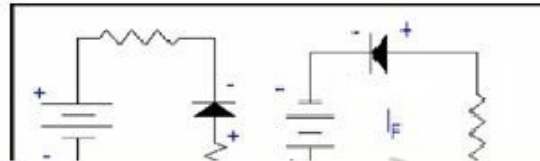
Given below are two figures (a) and (b) having Diode, In which diode current will flow and will not flow? Give its reason.



Answer ( Please [click here](#) to Add Answer )

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

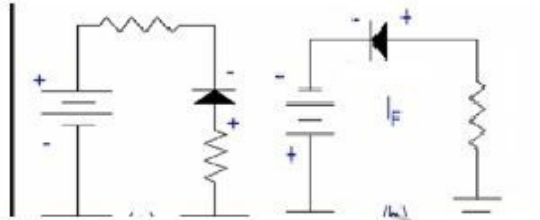
**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Answer ( Please [click here](#) to Add Answer )

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

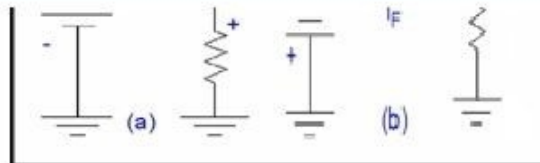CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM



Answer ( Please [click here](#) to Add Answer )




**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



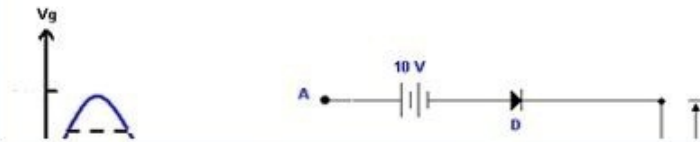Tell the name of circuit in fig (b) and how it response for input signal of fig. (a)?



Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**


**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**


**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

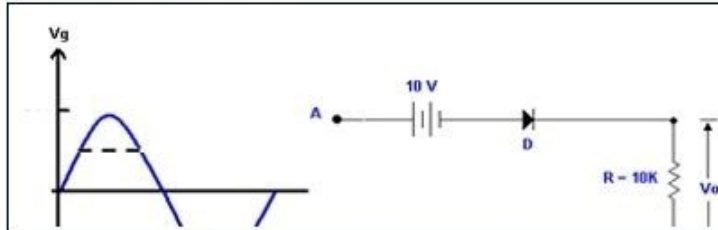

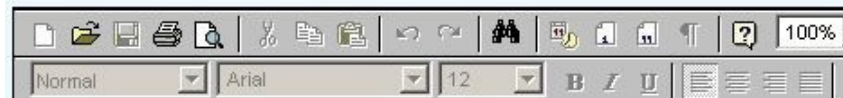Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

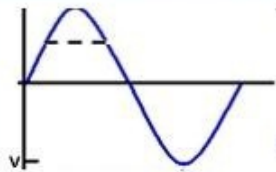


Fig (a)

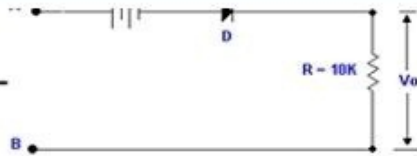


Fig (b)

Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**


**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

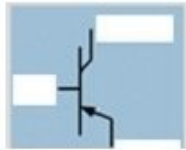**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Label the given diagram for transistor symbol and write its type as well.



Answer ( Please [click here](#) to Add Answer )




**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



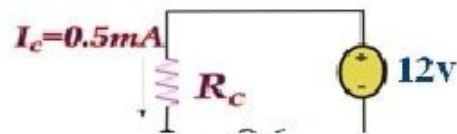For the circuit shown, find  $I_E$  &  $R_C$




Answer ( Please [click here](#) to Add Answer )



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

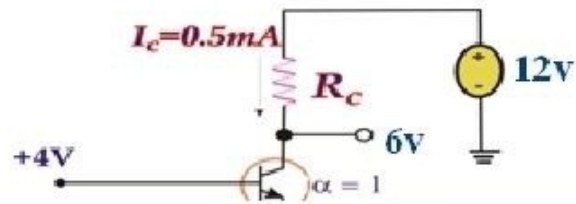CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM






Answer ( Please [click here](#) to Add Answer )

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

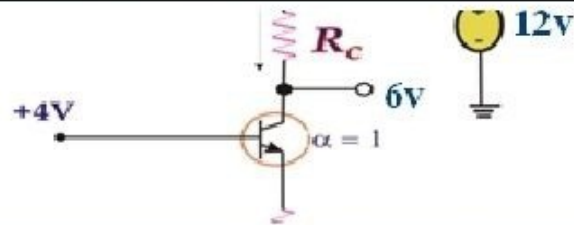CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM



Answer ( Please [click here](#) to Add Answer )

CORRECT ANSWER SOLVED BY HADI


CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

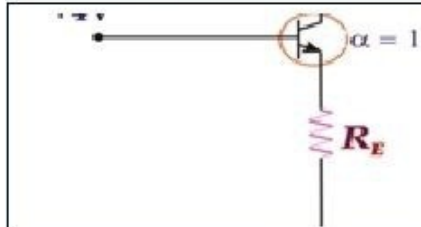

Answer ( Please [click here](#) to Add Answer )

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI

CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM



Answer ( Please [click here](#) to Add Answer )


CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

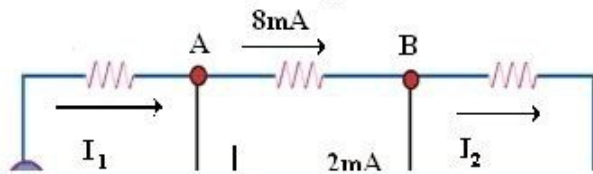Calculate the values of  $I_1$  and  $I_2$ .



Answer ( Please [click here](#) to Add Answer )


CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306

EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM



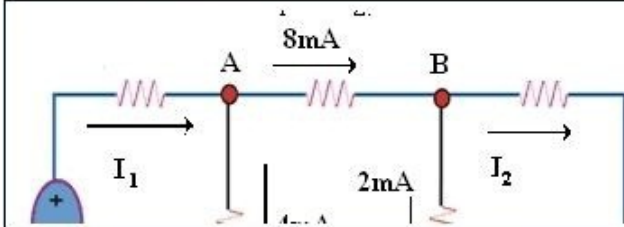


Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

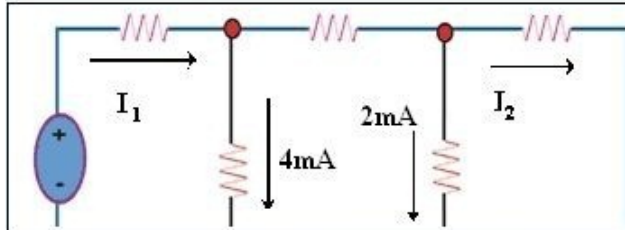**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**




Answer ( Please [click here](#) to Add Answer )



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

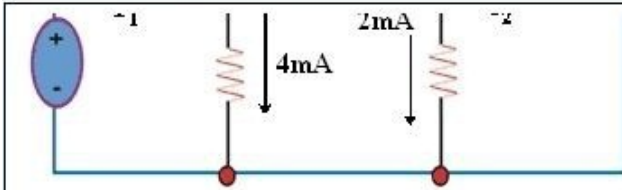CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM



Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**


**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

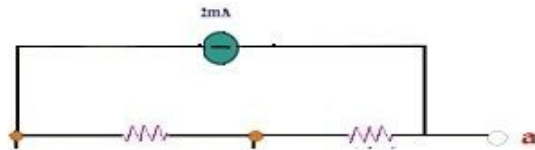**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Using the **Thevenin's Theorem**, find Thevenin's Resistance  $R_{th}$  to the left of a,b . Draw the circuit.




Answer ( Please [click here](#) to Add Answer )



CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM

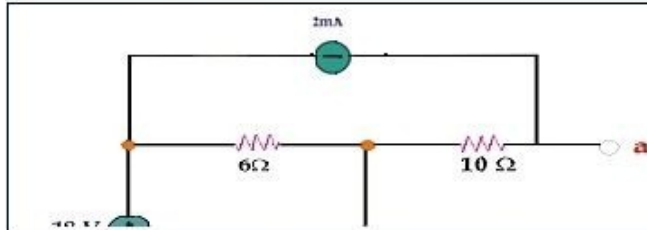CORRECT ANSWER SOLVED BY HADI  
CELL NO: 03228043306  
EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM



Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**


**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



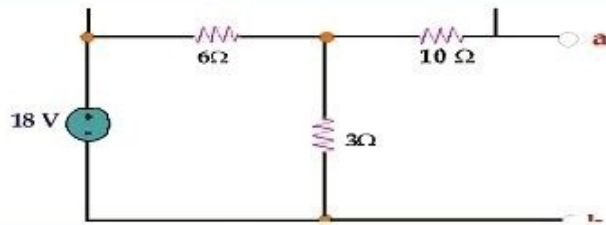


Answer ( Please [click here](#) to Add Answer )

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

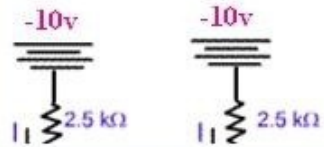Find the value of current  $I$  and voltage  $V$  in the circuits shown in figure (a) and (b). (Assuming the diodes to be ideal).



Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**


**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**


**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

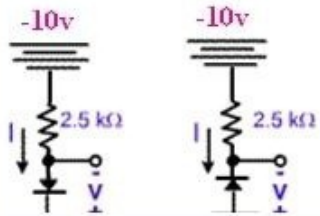

Answer ( Please [click here](#) to Add Answer )

**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

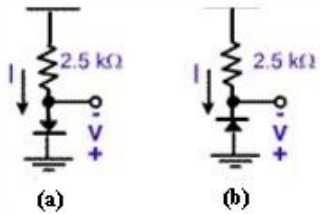**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

Answer ( Please [click here](#) to Add Answer )



**CORRECT ANSWER SOLVED BY HADI**  
**CELL NO: 03228043306**  
**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**



Find the value of the diode small signal resistance  $r_d$  at bias current of 0.1mA and 10mA. Assume  $n=1$

Answer ( Please [click here](#) to Add Answer )

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**

**CORRECT ANSWER SOLVED BY HADI**

**CELL NO: 03228043306**

**EMAIL: HADIRAJPUTOFFICIAL@GMAIL.COM**