

بِسْمِ اللَّهِ الرَّحْمَنِ الرَّحِيمِ

کیا آپ نے آج درود شریف پڑھا

نہیں تو ابھی پڑھ لیجئے

صلی اللہ علیہ وسلم

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَيْسَ

عَمَّ

الْمَصَّ

أَمِين

ق

كَأَيِّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!



VU Stars

اسلام علیکم:

امید کرتا ہوں سب خیریت سے ہوں گئے۔ آنے والے تمام نیو طالب علم کو میں ورچوئل یونیورسٹی آف پاکستان میں خوش آمدید کرتا ہوں۔
اگر کسی سٹوڈنٹ کو کسی بھی قسم کی ہیلپ چاہے ہو تو ہم سے رابطہ کر سکتا ہے جیسا کہ: پاسٹ پیپرز، کورس سلیکشن، پروجیکٹ سلیکشن، ڈیٹ شیٹ،
فیس پے اور چینج سٹڈی پروگرام وغیرہ۔

Paid

VU LMS

اگر کوئی سٹوڈنٹ کسی مجبوری کی وجہ سے یا جاب ہو لڈز ہونے کی وجہ سے اپنا ایل ایم ایس خود ہینڈل نہیں کر سکتا تو وہ ہم سے پیڈ سروس حاصل کر
سکتا ہے کوشش کرے کے آپ ہر چیز خود اٹیمپٹ کریں اگر نہیں کر سکتے تو سروس حاصل کریں۔

Email:

waqasahmeduog@gmail.com

انشاء اللہ آپ ہماری سروس سے مطمئن ہوں گے۔

Whatsapp: 03066295623

مزید اگر کسی رہنمائی کی ضرورت ہو تو وہ رابطہ کر سکتا ہے۔

Question # 6 of 10 (Start time: 05:19:53 PM, 26 August 2022)

State of flip-flop can be switched by changing its_____.

Select the correct option

☐	Momentary Signal
☐	Contemporary Signal
☒	Input Signal
☐	Output Signal

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 05:20:09 PM, 26 August 2022)

To implement the counter using S-R flip-flops instead of J-K flip-flops, the _____ transition table is used.

Select the correct option

☐	Next State
☐	J-K
☐	None of above
☒	S-R

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:20:26 PM, 26 August 2022)

The 3-bit up counter can be implemented using _____ flip-flop(s).

Select the correct option

☐	S-R Flip-flops Only
☐	D-Flip-flop Only
☐	S-R Flip-flops or D-Flip-flops
☒	S-R Flip-flops and D-Flip-flops

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 05:20:53 PM, 26 August 2022)

A decade counter is -----

Select the correct option

☒	Mod-10 counter
☐	Mod-8 counter
☐	Mod-3 counter
☐	Mod-5 counter

Waqas Ahmed: 0306-6295623

Question # 10 of 10 (Start time: 05:21:03 PM, 26 August 2022)

The power consumed by a flip-flop is defined by _____

Select the correct option

☐	$P = I_{cc} \times R_{cc}$
☐	$P = M_{cc} \times V_{cc}$
☐	$P = V_{cc} \times R_{cc}$
☒	$P = V_{cc} \times I_{cc}$

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 05:26:26 PM, 26 August 2022)

In gated SR latch, what is the value of the output if $EN=1$, $S=0$ and $R=1$?

Select the correct option

☒	0
☐	Invalid
☐	Qt
☐	1

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 05:26:39 PM, 26 August 2022)

The _____ inputs can be directly mapped to Karnaugh maps.

Select the correct option

☐	External
☐	S-R
☐	Flip-flop
☒	J-K

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 05:26:59 PM, 26 August 2022)

When the _____ Hz sampling interval is selected, the signal at the output of the J-K flip-flop has a time period of _____ second

Select the correct option

☐	2,5
☐	0,2
☐	1,1
☒	1,2

Waqas Ahmed: 0306-6295623

Question # 4 of 10 (Start time: 05:27:13 PM, 26 August 2022)

In moore machine the output depends on

Select the correct option

☐	the current state and the output of previous flip flop
☐	only inputs
☒	the current state
☐	the current state and inputs

Waqas Ahmed: 0306-6295623



VU Stars

اسلام علیکم:

امید کرتا ہوں سب خیریت سے ہوں گئے۔ آنے والے تمام نیو طالب علم کو میں ورچوئل یونیورسٹی آف پاکستان میں خوش آمدید کرتا ہوں۔
اگر کسی سٹوڈنٹ کو کسی بھی قسم کی ہیلپ چاہے ہو تو ہم سے رابطہ کر سکتا ہے جیسا کہ: پاسٹ پیپرز، کورس سلیکشن، پروجیکٹ سلیکشن، ڈیٹ شیٹ،
فیس پے اور چینج سٹڈی پروگرام وغیرہ۔

Paid

VU LMS

اگر کوئی سٹوڈنٹ کسی مجبوری کی وجہ سے یا جاب ہو لڈر ہونے کی وجہ سے اپنا ایل ایم ایس خود ہینڈل نہیں کر سکتا تو وہ ہم سے پیڈ سروس حاصل کر
سکتا ہے کوشش کرے کے آپ ہر چیز خود اٹیمپٹ کریں اگر نہیں کر سکتے تو سروس حاصل کریں۔

Email:

waqasahmeduog@gmail.com

انشاء اللہ آپ ہماری سروس سے مطمئن ہوں گے۔

Whatsapp: 03066295623

مزید اگر کسی رہنمائی کی ضرورت ہو تو وہ رابطہ کر سکتا ہے۔

Question # 4 of 10 (Start time: 05:27:13 PM, 26 August 2022)

In moore machine the output depends on

Select the correct option

☐	the current state and the output of previous flip flop
☐	only inputs
☒	the current state
☐	the current state and inputs

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 05:27:32 PM, 26 August 2022)

RCO stands for _____

Select the correct option

☐	Reconfiguration Clock Output
☒	Ripple Clock Output
☐	Reconfiguration Counter Output
☐	Ripple Counter Output

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 05:27:43 PM, 26 August 2022)

In case of cascading Integrated Circuit counters, the enable inputs and RCO of the Integrated Circuit counters allow cascading

Select the correct option

False



Waqas Ahmed: 0306-6295623

True



Question # 7 of 10 (Start time: 05:27:58 PM, 26 August 2022)

A flip-flop is connected to +5 volts and it draws 5 mA of current during its operation, the power dissipation of the flip-flop is

Select the correct option

☒	25 mW
☐	10 mW
☐	1024 mW
☐	64 mW

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:28:16 PM, 26 August 2022)

Design of state diagram is one of many steps used to design

Select the correct option

☐	a clock
☒	any counter
☐	a truncated counter
☐	an UP/DOWN counter

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 05:28:25 PM, 26 August 2022)

A decade counter can be implemented by truncating the counting sequence of a MOD-20 counter.

Select the correct option

False

☐

Waqas Ahmed: 0306-6295623

True

☒

Question # 10 of 10 (Start time: 05:28:33 PM, 26 August 2022)

In designing any counter the transition from a current state to the next state is determined by

Select the correct option

☒	Current state and inputs
☐	Only current state
☐	Only inputs
☐	current state and outputs

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 05:30:25 PM, 26 August 2022)

The minimum time required for the input logic levels to remain stable before the clock transition occurs is known as the _ _ _ _ _

Select the correct option

☒	Set-up time
☐	Pulse Stability time (PST)
☐	Hold time
☐	Pulse Interval time

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 2 of 10 (Start time: 05:30:41 PM, 26 August 2022)

An Asynchronous Down-counter is implemented (Using J-K flip-flop) by connecting -----

Select the correct option

☒	Q output of all flip-flops to clock input of next flip-flops
☐	Q' output of all flip-flops to K input of next flip-flops
☐	Q' output of all flip-flops to clock input of next flip-flops
☐	Q output of all flip-flops to J input of next flip-flops

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 05:31:10 PM, 26 August 2022)

_____ is one of the examples of asynchronous inputs.

Select the correct option

☐	J-K input
☒	Clear Input (CLR)
☐	D input
☐	S-R input

Waqas Ahmed: 0306-6295623

Question # 4 of 10 (Start time: 05:31:20 PM, 26 August 2022)

The glitches due to "Race Condition" can be avoided by using a _____

Select the correct option

☐	Gated flip-flops
☐	Positive-Edge triggered flip-flops
☐	Pulse triggered flip-flops
☒	Negative-Edge triggered flip-flops

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 05:31:40 PM, 26 August 2022)

Karnaugh map is used in designing

Select the correct option

☒	All of the above
☐	a counter
☐	a clock
☐	an UP/DOWN counter

Waqas Ahmed: 0306-6295623



VU Stars

اسلام علیکم:

امید کرتا ہوں سب خیریت سے ہوں گئے۔ آنے والے تمام نیو طالب علم کو میں ورچوئل یونیورسٹی آف پاکستان میں خوش آمدید کرتا ہوں۔
اگر کسی سٹوڈنٹ کو کسی بھی قسم کی ہیلپ چاہے ہو تو ہم سے رابطہ کر سکتا ہے جیسا کہ: پاسٹ پیپرز، کورس سلیکشن، پروجیکٹ سلیکشن، ڈیٹ شیٹ،
فیس پے اور چینج سٹڈی پروگرام وغیرہ۔

Paid

VU LMS

اگر کوئی سٹوڈنٹ کسی مجبوری کی وجہ سے یا جاب ہو لڈر ہونے کی وجہ سے اپنا ایل ایم ایس خود ہینڈل نہیں کر سکتا تو وہ ہم سے پیڈ سروس حاصل کر
سکتا ہے کوشش کرے کے آپ ہر چیز خود اٹھپیٹ کریں اگر نہیں کر سکتے تو سروس حاصل کریں۔

Email:

waqasahmeduog@gmail.com

انشاء اللہ آپ ہماری سروس سے مطمئن ہوں گے۔

Whatsapp: 03066295623

مزید اگر کسی رہنمائی کی ضرورت ہو تو وہ رابطہ کر سکتا ہے۔

Question # 6 of 10 (Start time: 05:31:51 PM, 26 August 2022)

If $S=1$ and $R=1$, for negative edge triggered flip-flop then
 $Q(t+1) = \text{-----}$

Select the correct option

☐	Input is invalid
☐	1
☒	Invalid
☐	0

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 05:33:17 PM, 26 August 2022)

A positive edge-triggered flip-flop changes its state when -----

Select the correct option

☐	Preset input (PRE) is set
☐	High-to-low transition of clock
☐	Enable input (EN) is set
☒	Low-to-high transition of clock

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:33:33 PM, 26 August 2022)

The operation of J-K flip-flop is similar to that of the SR flip-flop except that the J-K flip-flop -----

Select the correct option

☐	It does not accept asynchronous inputs
☐	It does not show transition on change in pulse
☐	Sets to clear when both $J = 0$ and $K = 0$
☒	Doesn't have an invalid state

Waqas Ahmed: 0306-6295623



Question # 9 of 10 (Start time: 05:33:55 PM, 26 August 2022)

A mono-stable device only has a single stable state

Select the correct option

True



Waqas Ahmed: 0306-6295623

False



Question # 10 of 10 (Start time: 05:34:03 PM, 26 August 2022)

The terminal count of a 4-bit binary counter in the DOWN mode is _____

Select the correct option

☒	0000
☐	0011
☐	1100
☐	1111

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 05:36:36 PM, 26 August 2022)

_____ is one of the examples of asynchronous inputs.

Select the correct option

☐	D input
☒	Clear Input (CLR)
☐	S-R input
☐	J-K input

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 05:36:44 PM, 26 August 2022)

when the transmission line is idle in an asynchronous transmission

Select the correct option

☒	It is set to logic high
☐	It remains in previous state
☐	It is set to logic low
☐	State of transmission line is not used to start transmission

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 05:37:05 PM, 26 August 2022)

When the _____ Hz sampling interval is selected, the signal at the output of the J-K flip-flop has a time period of _____ second

Select the correct option

☐	0,2
☐	2,5
☐	1,1
☒	1,2

Waqas Ahmed: 0306-6295623



VU Stars

اسلام علیکم:

امید کرتا ہوں سب خیریت سے ہوں گئے۔ آنے والے تمام نیو طالب علم کو میں ورچوئل یونیورسٹی آف پاکستان میں خوش آمدید کرتا ہوں۔
اگر کسی سٹوڈنٹ کو کسی بھی قسم کی ہیلپ چاہے ہو تو ہم سے رابطہ کر سکتا ہے جیسا کہ: پاسٹ پیپرز، کورس سلیکشن، پروجیکٹ سلیکشن، ڈیٹ شیٹ،
فیس پے اور چینج سٹڈی پروگرام وغیرہ۔

Paid

VU LMS

اگر کوئی سٹوڈنٹ کسی مجبوری کی وجہ سے یا جاب ہو لڈر ہونے کی وجہ سے اپنا ایل ایم ایس خود ہینڈل نہیں کر سکتا تو وہ ہم سے پیڈ سروس حاصل کر
سکتا ہے کوشش کرے کے آپ ہر چیز خود اٹیمپٹ کریں اگر نہیں کر سکتے تو سروس حاصل کریں۔

Email:

waqasahmeduog@gmail.com

انشاء اللہ آپ ہماری سروس سے مطمئن ہوں گے۔

Whatsapp: 03066295623

مزید اگر کسی رہنمائی کی ضرورت ہو تو وہ رابطہ کر سکتا ہے۔

Question # 4 of 10 (Start time: 05:37:15 PM, 26 August 2022)

A negative edge-triggered flip-flop changes its state when -----

Select the correct option

☒	High-to-low transition of clock
☐	Low-to-high transition of clock
☐	Preset input (PRE) is set
☐	Enable input (EN) is set

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 05:38:08 PM, 26 August 2022)

If the S and R inputs of the gated S-R latch are connected together using a _____ gate then there is only a single input to the latch (A gated D-Latch)

Select the correct option

☐	OR
☐	AND
☒	NOT
☐	XOR

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 6 of 10 (Start time: 05:38:40 PM, 26 August 2022)

A-stable multi-vibrator continuously changes from one unstable state to the other without any_____.

▶ Select the correct option

☐	External trigger
☐	Variable
☐	Flip flop
☐	Output

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 05:38:40 PM, 26 August 2022)

A-stable multi-vibrator continuously changes from one unstable state to the other without any_____.

Select the correct option

☒	External trigger
☐	Variable
☐	Flip flop
☐	Output

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 05:40:13 PM, 26 August 2022)

Karnaugh map is used in designing

Select the correct option

☐	a clock
☐	a counter
☒	All of the above
☐	an UP/DOWN counter

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 05:41:33 PM, 26 August 2022)

In Master-Slave flip-flop the Clock signal is connected to Slave flip-flop using _____ gate

Select the correct option

☐	OR
☐	AND
☒	NOT
☐	NAND

Waqas Ahmed: 0306-6295623

Question # 10 of 10 (Start time: 05:41:52 PM, 26 August 2022)

the terminal count of a modulus-13 binary counter is

Select the correct option

☐	1100
☐	0000
☒	1101
☐	1111

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 05:47:50 PM, 26 August 2022)

The 74HC163 is a 4-bit Synchronous Counter.it has.....parallel data inputs pins

Select the correct option

☐	8
☐	6
☐	2
☒	4

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 05:48:11 PM, 26 August 2022)

In case of cascading Integrated Circuit counters, the enable inputs and RCO of the Integrated Circuit counters allow cascading

Select the correct option

False



Waqas Ahmed: 0306-6295623

True



Question # 3 of 10 (Start time: 05:48:20 PM, 26 August 2022)

In asynchronous digital systems all the circuits change their state with respect to a common clock

Select the correct option

False



Waqas Ahmed: 0306-6295623

True



Question # 4 of 10 (Start time: 05:48:34 PM, 26 August 2022)

Divide-by-160 counter is achieved by using

Select the correct option

☐	DIV 16 and DIV 32
☐	Flip-Flop and DIV 10
☒	DIV 16 and DIV 10
☐	Flip-Flop and DIV 16

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 05:50:10 PM, 26 August 2022)

Asynchronous mean that_____

Select the correct option

☐	Each alternative flip-flop after the first one is enabled by the output of the preceding flip-flop
☒	Each flip-flop after the first one is enabled by the output of the preceding flip-flop
☐	Each flip-flop is enabled by the output of the preceding flip-flop
☐	Each flip-flop except the last one is enabled by the output of the preceding flip-flop

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 05:50:37 PM, 26 August 2022)

In Master-Slave flip-flop the Clock signal is connected to Slave flip-flop using _____ gate

Select the correct option

☒	NOT
☐	OR
☐	AND
☐	NAND

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:50:48 PM, 26 August 2022)

A transparent mode means -----

Select the correct option

☒	The changes in the data at the inputs of the latch are seen at the output
☐	Propagation Delay is zero (Output is immediately changed when clock signal is applied)
☐	Input Hold time is zero (no need to maintain input after clock transition)
☐	The changes in the data at the inputs of the latch are not seen at the output

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 05:51:11 PM, 26 August 2022)

With a 100 KHz clock frequency, eight bits can be serially entered into a shift register in

Select the correct option

☐	80 mili seconds
☐	8 micro seconds
☒	80 micro seconds
☐	10 micro seconds

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 05:54:38 PM, 26 August 2022)

We have a digital circuit. Different parts of circuit operate at different clock frequencies (4MHZ, 2MHZ and 1MHZ), but we have a 4MHZ clock source. To supply the required frequency to each part of circuit, we can get help by using -----

Select the correct option

☐	D-flipflop
☐	T-Flip-Flop
☐	Using S-R Flop-Flop
☒	J-K flip-flop

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 05:55:06 PM, 26 August 2022)

_____ is one of the examples of asynchronous inputs.

Select the correct option

☐	J-K input
☐	S-R input
☒	Clear Input (CLR)
☐	D input

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 05:55:19 PM, 26 August 2022)

A decade counter is _____

Select the correct option

☐	Mod-8 counter
☐	Mod-3 counter
☐	Mod-5 counter
☒	Mod-10 counter

Waqas Ahmed: 0306-6295623

Question # 4 of 10 (Start time: 05:55:28 PM, 26 August 2022)

A mono-stable device only has a single stable state

Select the correct option

True



Waqas Ahmed: 0306-6295623

False



لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 5 of 10 (Start time: 05:55:38 PM, 26 August 2022)

----- flip-flops are obsolete now.

Select the correct option

☐	D-Flipflop
☐	T-Flipflop
☒	Master-Slave
☐	Edge-triggered

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 05:56:35 PM, 26 August 2022)

For a gated D-Latch if $EN=1$ and $D=1$ then $Q(t+1) = \text{-----}$

Select the correct option

☐	0
☒	1
☐	$Q(t)$
☐	Invalid

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:56:46 PM, 26 August 2022)

_____occurs when the same clock signal arrives at different times at different clock inputs due to propagation delay.

Select the correct option

☒	Clock Skew
☐	None of given options
☐	Race condition
☐	Ripple Effect

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:56:46 PM, 26 August 2022)

_____occurs when the same clock signal arrives at different times at different clock inputs due to propagation delay.

Select the correct option

☒	Clock Skew
☐	None of given options
☐	Race condition
☐	Ripple Effect

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 05:57:02 PM, 26 August 2022)

If a circuit suffers "Clock Skew " problem, the output of circuit can't be guaranteed.

Select the correct option

False

☐

Waqas Ahmed: 0306-6295623

True

☒

Question # 10 of 10 (Start time: 05:57:21 PM, 26 August 2022)

A negative edge-triggered flip-flop changes its state when -----

Select the correct option

☐	Low-to-high transition of clock
☒	High-to-low transition of clock
☐	Preset input (PRE) is set
☐	Enable input (EN) is set

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 06:36:03 PM, 26 August 2022)

We have a digital circuit. Different parts of circuit operate at different clock frequencies (4MHZ, 2MHZ and 1MHZ), but we have a 4MHZ clock source. To supply the required frequency to each part of circuit, we can get help by using -----

Select the correct option

☐	T-Flip-Flop
☒	Using S-R Flop-Flop
☐	J-K flip-flop
☐	D-flipflop

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 06:36:29 PM, 26 August 2022)

A mono-stable device only has a single stable state

Select the correct option

True



Waqas Ahmed: 0306-6295623

False



Question # 3 of 10 (Start time: 06:36:47 PM, 26 August 2022)

The n flip-flops store _____ states.

Select the correct option

☐	0
☐	1
☐	$2^{(n+1)}$
☒	2^n

Waqas Ahmed: 0306-6295623

Question # 4 of 10 (Start time: 06:37:10 PM, 26 August 2022)

A negative edge-triggered flip-flop changes its state when -----

Select the correct option

☒	High-to-low transition of clock
☐	Low-to-high transition of clock
☐	Preset input (PRE) is set
☐	Enable input (EN) is set

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 5 of 10 (Start time: 06:37:19 PM, 26 August 2022)

Divide-by-160 counter is achieved by using

Select the correct option

☐	DIV 16 and DIV 32
☐	Flip-Flop and DIV 10
☒	DIV 16 and DIV 10
☐	Flip-Flop and DIV 16

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 06:37:31 PM, 26 August 2022)

In gated SR latch, what is the value of the output if $EN=1$, $S=0$ and $R=1$?

Select the correct option

☐	Invalid
☒	0
☐	Qt
☐	1

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 06:37:31 PM, 26 August 2022)

In gated SR latch, what is the value of the output if $EN=1$, $S=0$ and $R=1$?

Select the correct option

☐	Invalid
☒	0
☐	Qt
☐	1

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 06:37:54 PM, 26 August 2022)

State of flip-flop can be switched by changing its_____.

Select the correct option

☒	Input Signal
☐	Contemporary Signal
☐	Momentary Signal
☐	Output Signal

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 06:38:06 PM, 26 August 2022)

When the both inputs of edge-triggered J-K flop-flop are set to logic zero -----

Select the correct option

☐	Q=1 and Q'=0
☐	Q=0 and Q'=1
☒	The output of flip-flop remains unchanged
☐	The flop-flop is triggered

Waqas Ahmed: 0306-6295623

Question # 10 of 10 (Start time: 06:39:20 PM, 26 August 2022)

----- Counters as the name indicates are not triggered simultaneously

Select the correct option

☐	Negative-Edge triggered
☐	Positive-Edge triggered
☒	Synchronous
☐	Asynchronous

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 08:02:33 PM, 26 August 2022)

Three cascaded modulus-10 counters have an overall modulus of

Select the correct option

☐	30
☐	10000
☐	100
☒	1000

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 08:02:42 PM, 26 August 2022)

Flip flops are also called -----

Select the correct option

☒	Bi-stable multivibrators
☐	Bi-stable single vibrators
☐	Bi-stable transformer
☐	Bi-stable dual vibrators

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 08:02:53 PM, 26 August 2022)

The minimum time for which the input signal has to be maintained at the input of flip-flop is called _____ of the flip-flop.

Select the correct option

☐	Pulse Stability time (PST)
☐	Pulse Interval time
☐	Set-up time
☒	Hold time

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 08:03:47 PM, 26 August 2022)

Each stage of Master-slave flip-flop works at ____ of the clock signal

Select the correct option

☒	One half
☐	Each stage works on complete clock signal
☐	One third
☐	One fourth

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 6 of 10 (Start time: 08:04:11 PM, 26 August 2022)

A decade counter can be implemented by truncating the counting sequence of a MOD-20 counter.

Select the correct option

False



Waqas Ahmed: 0306-6295623

True



Question # 7 of 10 (Start time: 08:04:22 PM, 26 August 2022)

A-stable multi-vibrator continuously changes from one unstable state to the other without any_____.

Select the correct option

☒	External trigger
☐	Flip flop
☐	Output
☐	Variable

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 08:04:30 PM, 26 August 2022)

The 74HC163 is a 4-bit Synchronous Counter.it has.....parallel data inputs pins

Select the correct option

☐	2
☐	8
☒	4
☐	6

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 08:04:49 PM, 26 August 2022)

RCO stands for _____

Select the correct option

☐	Reconfiguration Clock Output
☒	Ripple Clock Output
☐	Ripple Counter Output
☐	Reconfiguration Counter Output

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 08:06:57 PM, 26 August 2022)

A Divide-by-20 counter can be achieved by using

Select the correct option

☐	Flip-Flop and DIV 32
☐	Div 10 and DIV 16
☒	Flip-Flop and DIV 10
☐	Flip-Flop and DIV 16

Waqas Ahmed: 0306-6295623

Question # 2 of 10 (Start time: 08:07:11 PM, 26 August 2022)

In gated SR latch, what is the value of the output if $EN=1$, $S=0$ and $R=0$?

Select the correct option

☐	0
☐	Q_t
☐	Invalid
☒	1

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 08:07:21 PM, 26 August 2022)

when the transmission line is idle in an asynchronous transmission

Select the correct option

☐	State of transmission line is not used to start transmission
☐	It is set to logic low
☒	It is set to logic high
☐	It remains in previous state

Waqas Ahmed: 0306-6295623

Question # 4 of 10 (Start time: 08:07:34 PM, 26 August 2022)

A synchronous decade counter will have _____ flip-flops

Select the correct option

☐	7
☐	3
☒	4
☐	10

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 08:07:41 PM, 26 August 2022)

In case of cascading Integrated Circuit counters, the enable inputs and RCO of the Integrated Circuit counters allow cascading

Select the correct option

False



Waqas Ahmed: 0306-6295623

True



لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَيْسَ

عَمَّ

الْمَصَّ

أَمِين

ق

كَأَيِّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 6 of 10 (Start time: 08:07:50 PM, 26 August 2022)

A one-shot mono-stable device contains -----

Select the correct option

☐	NAND gate, Resistor, Capacitor and NOT Gate
☐	AND gate, Resistor, Capacitor and NOT Gate
☐	XNOR gate, Resistor, Capacitor and NOT Gate
☒	NOR gate, Resistor, Capacitor and NOT Gate

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 08:08:11 PM, 26 August 2022)

_____ is one of the examples of asynchronous inputs.

Select the correct option

☐	S-R input
☒	Clear Input (CLR)
☐	J-K input
☐	D input

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 08:08:23 PM, 26 August 2022)

When the _____ Hz sampling interval is selected, the signal at the output of the J-K flip-flop has a time period of _____ second

Select the correct option

☐	2,5
☐	1,1
☐	0,2
☒	1,2

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 08:08:34 PM, 26 August 2022)

A flip-flop is presently in SET state and must remain SET on the next clock pulse. What must j and K be?

Select the correct option

☐	J = 1, K = 0
☐	J = 0, K = X(Don't care)
☒	J = X(Don't care), K = 0
☐	J = 1, K = X(Don't care)

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 02:22:39 PM, 30 August 2022)

When did Yahya Khan hand over power to Zulfiqar Ali Bhutto?

Select the correct option



20th December, 1971



20th October, 1971

Waqas Ahmed: 0306-6295623



20th November, 1971



20th September, 1971

Question # 7 of 10 (Start time: 02:22:52 PM, 30 August 2022)

Who abrogated the 1956 Constitution of Pakistan?

Select the correct option

☐	Yahya Khan
☐	Tikka Khan
☒	Iskandar Mirza
☐	Ayub Khan

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 02:23:03 PM, 30 August 2022)

What was the duration of second term of Benazir Bhutto's Government?

Select the correct option



October 1993–November 1996



October 1991–November 1992

Waqas Ahmed: 0306-6295623



October 1995–November 1998



October 1983–November 1986

Question # 9 of 10 (Start time: 02:23:23 PM, 30 August 2022)

Pakistan Peoples Party won_____ number of seats in general elections of 1970.

Select the correct option

☐	92
☐	89
☒	81
☐	98

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 02:27:49 PM, 30 August 2022)

Who was the interim Prime Minister during the period of April-May 1993?

Select the correct option

☐	Ghulam Mustafa Jatoi
☐	Dr. Moeen Qureshi
☒	Balakh Sher Mazari
☐	Malik Meraj Khalid

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 02:28:57 PM, 30 August 2022)

Where are the deposits of Sulphur found in Pakistan?

Select the correct option

☐	Jhelum, Mianwali, Attock
☒	Kalat, Khairpur, Mardan
☐	Deegari, Sharig, Soer
☐	Thatta, Tharparkar, Manara

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 02:29:14 PM, 30 August 2022)

Line of Control (LOC) is a boundary between Pakistan and _____.

Select the correct option

☐	China
☐	Afghanistan
☐	Iran
☒	India

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 02:29:28 PM, 30 August 2022)

According to 1973 Constitution, Pakistan had a _____.

Select the correct option

☐	Tricameral Parliament
☐	Multicameral Parliament
☒	Unicameral Parliament
☐	Bicameral Parliament

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَيْسَ

عَمَّ

الْمَصَّ

أَمِين

ق

كَأَيِّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 8 of 10 (Start time: 02:29:39 PM, 30 August 2022)

What was the status of the 1973 Constitution during 1977 – 1985?

Select the correct option

☐	Operational after changes
☐	Operational
☒	Suspended
☐	Abrogated

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 02:29:51 PM, 30 August 2022)

When Usher was imposed on agriculture products?

Select the correct option

☐	1981
☐	1980
☐	1982
☒	1983

Waqas Ahmed: 0306-6295623



Question # 2 of 10 (Start time: 05:11:29 PM, 26 August 2022)

----- Counters as the name indicates are not triggered simultaneously

Select the correct option

☒	Asynchronous
☐	Positive-Edge triggered
☐	Negative-Edge triggered
☐	Synchronous

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 05:11:58 PM, 26 August 2022)

A transparent mode means -----

Select the correct option

☐	Propagation Delay is zero (Output is immediately changed when clock signal is applied)
☒	The changes in the data at the inputs of the latch are seen at the output
☐	The changes in the data at the inputs of the latch are not seen at the output
☐	Input Hold time is zero (no need to maintain input after clock transition)

Waqas Ahmed: 0306-6295623

Question # 4 of 10 (Start time: 05:12:24 PM, 26 August 2022)

If data is brought into the J terminal and its complement to the K terminal, a J-K flip-flop operates as a(n) _____.

Select the correct option

☐	N flip-flop
☐	S-C flip-flop
☐	S-R flip-flop
☒	D flip-flop

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 05:13:21 PM, 26 August 2022)

A stage in the shift register consists of

Select the correct option

☒	a flip flop
☐	a latch
☐	a byte of storage
☐	four bits of storage

Waqas Ahmed: 0306-6295623

Question # 6 of 10 (Start time: 05:13:33 PM, 26 August 2022)

_____ is one of the examples of synchronous inputs.

Select the correct option

☐	Clear Input (CLR)
☒	J-K input
☐	Preset input (PRE)
☐	EN input

Waqas Ahmed: 0306-6295623

Question # 7 of 10 (Start time: 05:13:59 PM, 26 August 2022)

With a 100 KHz clock frequency, eight bits can be serially entered into a shift register in

Select the correct option

☐	80 mili seconds
☐	8 micro seconds
☐	10 micro seconds
☒	80 micro seconds

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:14:22 PM, 26 August 2022)

_____ is one of the examples of asynchronous inputs.

Select the correct option

☒	J-K input
☐	Clear Input (CLR)
☐	S-R input
☐	D input

Waqas Ahmed: 0306-6295623

Question # 8 of 10 (Start time: 05:14:22 PM, 26 August 2022)

_____ is one of the examples of asynchronous inputs.

Select the correct option

☐	J-K input
☒	Clear Input (CLR)
☐	S-R input
☐	D input

Waqas Ahmed: 0306-6295623

Question # 9 of 10 (Start time: 05:15:37 PM, 26 August 2022)

Design of state diagram is one of many steps used to design

Select the correct option

☐	an UP/DOWN counter
☐	a truncated counter
☒	any counter
☐	a clock

Waqas Ahmed: 0306-6295623

Question # 10 of 10 (Start time: 05:15:55 PM, 26 August 2022)

The 74HC163 is a 4-bit Synchronous Counter.it has.....data output pins

Select the correct option

☐	2
☒	4
☐	8
☐	6

Waqas Ahmed: 0306-6295623

Question # 1 of 10 (Start time: 05:17:38 PM, 26 August 2022)

For a down counter that counts from (111 to 000), if current state is "101" the next state will be _____

Select the correct option

☐	111
☐	110
☐	010
☒	none of given options

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!

Question # 2 of 10 (Start time: 05:18:02 PM, 26 August 2022)

The minimum time for which the input signal has to be maintained at the input of flip-flop is called _____ of the flip-flop.

Select the correct option

☐	Pulse Interval time
☐	Set-up time
☐	Pulse Stability time (PST)
☒	Hold time

Waqas Ahmed: 0306-6295623

Question # 3 of 10 (Start time: 05:18:18 PM, 26 August 2022)

Divide-by-160 counter is achieved by using

Select the correct option

☐	Flip-Flop and DIV 16
☐	DIV 16 and DIV 32
☐	Flip-Flop and DIV 10
☒	DIV 16 and DIV 10

Waqas Ahmed: 0306-6295623

Question # 5 of 10 (Start time: 05:19:38 PM, 26 August 2022)

The term hold always means _____.

Select the correct option

☐	$Q=0, Q^{\bar{}}=1$
☐	$Q=1, Q^{\bar{}}=0$
☐	$Q=0, Q^{\bar{}}=0$
☒	No change

Waqas Ahmed: 0306-6295623

لوح قرآنی

ن

حَمْدُكَ

الْحَمْدُ

لَیْسَ

عَمَّ

الْمَصَّ

أَمِینَ

ق

كَلَّعَصَّ

AR PRINTERS
0321-9660987

اس کے دیکھنے والوں کی سب مشکلیں آسان ہو جائیں گی صبح اس کو دیکھ کر جو کام شروع کیا جائیگا پورا ہوگا اور غیبی طریقوں سے رزق آنے لگے گا!