

VIRTUAL UNIVERSITY OF PAKISTAN

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

TEAM HADI(VU LAHORE)

MID TERM PAST PAPER

We Deal All Kind of VU Project
(PHP, .NET, ANDROID, PYTHON)

MADE AND SOLVED BY HADI

WARNING: Team HADI is not responsible for any mistake or wrong answer. All students reading and using this document may check and confirm the answers at their own.



WhatsApp: 03087122922



FACEBOOK ID: <https://www.facebook.com/hadipastpapers/>

Best of luck!



Question # 2 of 30 (Start time: 10:23:55 PM, 28 December 2020)

Total Marks: 1

_____ have Buffers at the inputs which produce the actual variable and its complement.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

Select the correct option

☐	EPROM
☒	PAL
☐	PLA
☐	GAL

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 1 of 30 (Start time: 02:34:57 PM, 28 December 2020)

Total Marks: 1

In iterative circuit implementation of $A=B$ function, If input A_0 is equal to input B_0 , the ____ gate output in Module 0 is a 1 which is passed on to Module 1 through its Cascading input.

Select the correct option

☐	OR	
☐	XOR	
☐	NOR	
☒	XNOR	←

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 2 of 30 (Start time: 02:35:59 PM, 28 December 2020)

Total Marks: 1

_____ is invalid number of cells in a single group formed by the adjacent cells in K-map

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

Select the correct option

☐	2	
☐	8	
☒	12	
☐	16	



MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 28 of 30 (Start time: 02:59:13 PM, 28 December 2020)

Total Marks: 1

The _____ is the slowest and consumes more power.

Select the correct option

☒	Standard TTL	
☐	Schottky TTL	
☐	Advanced Schottky TTL	
☐	Low-Power Schottky TTL	

MADE BY HADIEmail: hadirainutofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 24 of 30 (Start time: 02:56:00 PM, 28 December 2020)

Total Marks: 1

8-bit parallel data can be converted into serial data by using _____ multiplexer

Select the correct option

☐	4-to-2	
☐	4-to-4	
☒	8-to-1	←
☐	8-to-4	

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 9 of 30 (Start time: 10:29:28 PM, 28 December 2020)

Total Marks

The measurable values generally change over a _____.

Select the correct option

☐	Specific period	//
☐	Discrete range	//
☐	Time	
☒	Continuous range	

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122922 (Team Hadi Lahore)

Question # 29 of 30 (Start time: 10:43:53 PM, 28 December 2020)

Total Marks

The Quine-McCluskey method has _____ number of steps.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Select the correct option

☒

2

☐

3

☐

4

☐

5

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 8 of 30 (Start time: 10:28:36 PM, 28 December 2020)

Total Marks: 1

For a Standard SOP expression, a _____ is placed in the cell corresponding to the product term (Minterm) present in the expression.

Select the correct option

☐	0	
☒	1	
☐	X (don't care condition)	
☐	Any of given option depending on SOP term.	

MADE BY HADIEmail: hadiqaiputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 21 of 30 (Start time: 10:39:19 PM, 28 December 2020)

Total Marks: 1

A _____ can not operate without a memory element.

Select the correct option

☐	cell
☒	counter
☐	clock
☐	unit

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question # 27 of 30 (Start time: 10:42:58 PM, 28 December 2020)

Total Marks:

The AND Gate performs a logical _____ function

Select the correct option

☐	Addition
☐	Subtraction
☒	Multiplication
☐	Division

MADE BY HADI

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question # 19 of 30 (Start time: 10:37:55 PM, 28 December 2020)

Total Marks

The ANSI/IEEE Standard 754 defines a _____ Single-Precision Floating Point format for binary numbers.

Select the correct option

☐	8-bit
☐	16-bit
☒	32-bit
☐	64-bit

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI

EMAIL:hadirajputofficial@gmail.com

WHATSAPP& CALL:03087122922

MADE BY HADI

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question # 16 of 30 (Start time: 10:35:56 PM, 28 December 2020)

Total Marks: 1

_____ is invalid number of cells in a single group formed by the adjacent cells in K-map

Select the correct option

☒	2	//
☐	8	//
☐	12	
☐	16	

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 4 of 30 (Start time: 02:37:46 PM, 28 December 2020)

Total Marks: 1

The below are Integrated Circuit Technologies except _____.

Select the correct option

☐	TTL
☐	ECL
☐	PMOS
☒	ETMOS

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 9 of 30 (Start time: 02:43:19 PM, 28 December 2020)

Total Marks: 1

A _____ is converted into a standard POS by using the rule $AA' = 0$.

Select the correct option

[Reload Math Equations](#)

☐	Non-standard SOP
☒	Non-standard POS
☐	Simplified SOP
☐	Simplified POS

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 11 of 30 (Start time: 02:44:46 PM, 28 December 2020)

Total Marks: 1

Boolean algebra is the _____ of Digital Systems.

Select the correct option

☐	Science
☒	Mathematics
☐	Expression
☐	Equation

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 11 of 30 (Start time: 10:30:31 PM, 28 December 2020)

Total Marks: 1

In 16-input multiplexer, the decoder inputs ____ and ____ enable one out of the four multiplexers.

Select the correct option

- | | |
|----------------------------------|------|
| ☐ | A, B |
| ☐ | B, C |
| ☒ | C, D |
| ☐ | A, D |

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 28 of 30 (Start time: 10:43:13 PM, 28 December 2020)

Total Marks: 1

The Programmable Array Logic (PAL) has _____ AND array and a _____ OR array.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

Select the correct option

- | | | |
|----------------------------------|-----------------------------|---|
| ☐ | Fixed, Programmable | / |
| ☒ | Programmable, Fixed | / |
| ☐ | Fixed, Fixed | |
| ☐ | Programmable , Programmable | |

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 6 of 30 (Start time: 10:26:53 PM, 28 December 2020)

Total Mark

A variable can have a ____ value.

Select the correct option

☐	0	
☐	1	
☒	0 or 1	
☐	0 and 1	

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 25 of 30 (Start time: 10:41:52 PM, 28 December 2020)

Total Marks: 1

The OR Gate performs a Boolean _____ function

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

Select the correct option

☒

Addition

☐

Subtraction

☐

Multiplication

☐

Division

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 12 of 30 (Start time: 10:31:09 PM, 28 December 2020)

Total Marks: 1

The boolean expression $X = AB + CD$ represents

Select the correct option

- | | | |
|----------------------------------|------------------------|----|
| ☐ | two ORs ANDed together | // |
| ☐ | a 4-input AND gate | // |
| ☒ | two ANDs ORed together | // |
| ☐ | an exclusive-Or | |

MADE BY HADIEmail: hadiraiputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 15 of 30 (Start time: 02:48:16 PM, 28 December 2020)

Total Marks: 1

A 5-variable karnaugh map has

Select the correct option

☐	Eight cells
☐	Sixteen cells
☒	Thirty two cells
☐	Sixty four cells

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922**MADE BY HADI**

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question # 18 of 30 (Start time: 10:37:29 PM, 28 December 2020)

Total Marks: 1

Inputs		Output
A	B	F
0	0	0
0	1	1
1	0	1
1	1	1

Select the correct option

☐	AND	//
☐	NOT	//
☒	OR	//
☐	XOR	

MADE BY HADIEmail: hadiraiputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 30 of 30 (Start time: 10:45:03 PM, 28 December 2020)

Total Marks: 1

In 16-bit ALU, the Carry Out 16 is generated only when ALU3 has received Carry In ____.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL-03087122922

Select the correct option

☐	2	
☐	4	
☐	8	
☒	12	

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 3 of 30 (Start time: 02:37:04 PM, 28 December 2020)

Total Marks: 1

The GAL16V8 has eight _____ each connected to eight product terms.

Select the correct option

☒	OLMCs
☐	SOP
☐	POS
☐	cells

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122922 (Team Hadi Lahore)

Question # 26 of 30 (Start time: 02:57:25 PM, 28 December 2020)

Total Marks: 1

A standard SOP form has _____ terms that have all the variables in the domain of the expression.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

Select the correct option

☐	Sum
☒	Product
☐	Max
☐	Composite

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 22 of 30 (Start time: 02:54:38 PM, 28 December 2020)

Total Marks: 1

Caveman number system is Base _____ number system

Select the correct option

☐	2	//
☒	5	//
☐	10	
☐	16	

MADE BY HADI

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question # 26 of 30 (Start time: 10:42:10 PM, 28 December 2020)

Total Marks: 1

The OLMC of the GAL16V8 is similar to the OLMC of the _____ with some enhancements.

Select the correct option

☒	GAL22V10	
☐	GAL16V10	
☐	GAL14V10	
☐	GAL12V10	

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 22 of 30 (Start time: 10:39:56 PM, 28 December 2020)

Total Marks: 1

A _____ attached to the Select inputs of the Demultiplexer routes the incoming serial bits to successive outputs where each bit is stored.

Select the correct option



memory



counter



buffer



data

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 6 of 30 (Start time: 02:39:50 PM, 28 December 2020)

Total Marks: 1

The Boolean expression $(A + B' + C)$ is

Select the correct option

☒	a sum term	//
☐	a literal term	//
☐	a product term	
☐	a minterm	

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 17 of 30 (Start time: 02:49:31 PM, 28 December 2020)

Total Marks: 1

Tri-State Buffer is a _____ gate with a control line that disconnects the output from the input.

Select the correct option

☐	OR
☐	AND
☐	NAND
☒	NOT

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122922 (Team Hadi Lahore)

Question # 13 of 30 (Start time: 02:46:36 PM, 28 December 2020)

Total Marks: 1

In 8-input multiplexer, the two outputs are connected through a/an _____ gate.

Select the correct option

☐	AND	
☒	OR	
☐	NOT	
☐	NOR	

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 14 of 30 (Start time: 02:47:12 PM, 28 December 2020)

Total Marks: 1

Which of the following is the MSI version of the Look-Ahead Carry Generator, which provides identical inputs and outputs except for the C4 output?

Select the correct option

- | | | |
|----------------------------------|---------|----|
| ☐ | 74XX180 | // |
| ☐ | 74XX181 | // |
| ☒ | 74XX182 | // |
| ☐ | 74XX183 | // |

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122922 (Team Hadi Lahore)

Question # 30 of 30 (Start time: 03:00:20 PM, 28 December 2020)

Total Marks: 1

When the error condition is not detected in BCD adder, the circuit output is 0 and the 2nd Adder input B is set to _____.

Select the correct option

☒	0000	/
☐	0001	/
☐	0010	/
☐	0011	/

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 16 of 30 (Start time: 02:49:06 PM, 28 December 2020)

Total Marks: 1

The 4-variable Karnaugh Map (K-Map) has _____ cells for min or max terms

Select the correct option

☐	4	
☐	8	
☐	12	
☒	16	

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 19 of 30 (Start time: 02:51:33 PM, 28 December 2020)

Total Marks: 1

In the Repeated-Division method, the Decimal number to be converted is divided by the _____.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

Select the correct option

- | | | |
|----------------------------------|---|----|
| ☒ | Base number | // |
| ☐ | 2 | // |
| ☐ | Maximum range value of target number system | // |
| ☐ | Minimum range value of target number system | |

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 15 of 30 (Start time: 10:33:57 PM, 28 December 2020)

Total Marks: 1

Adding two octal numbers "36" and "71" result in _____

Select the correct option

- | | | |
|----------------------------------|-----|----|
| ☐ | 213 | // |
| ☐ | 123 | // |
| ☒ | 127 | |
| ☐ | 345 | |

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 4 of 30 (Start time: 10:25:32 PM, 28 December 2020)

Total Marks: 1

The expression $F=A+B+C$ describes the operation of three bits ____ Gate.

Select the correct option

☒	OR
☐	AND
☐	NOT
☐	NAND

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922**MADE BY HADI**Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 23 of 30 (Start time: 02:55:22 PM, 28 December 2020)

Total Marks: 1

In 16-bit ALU, the Carry Out 16 is generated only when ALU3 has received Carry In ____.

Select the correct option

- | | |
|----------------------------------|----|
| ☐ | 2 |
| ☐ | 4 |
| ☐ | 8 |
| ☒ | 12 |

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 29 of 30 (Start time: 02:59:46 PM, 28 December 2020)

Total Marks: 1

A SOP expression having a domain of 3 variables will have a truth table having ____ combinations of inputs and corresponding output values.

Select the correct option

☒	2	
☐	4	
☐	8	
☐	16	

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL: 03087122922

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 10 of 30 (Start time: 02:44:20 PM, 28 December 2020)

Total Marks: 1

The Quine-McCluskey method has _____ number of steps.

Select the correct option

☒	2
☐	3
☐	4
☐	5

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 5 of 30 (Start time: 02:39:11 PM, 28 December 2020)

Total Marks: 1

To determine the seven expressions for each of the seven outputs in 7-segment display, seven ____-variable Karnaugh maps are used.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Select the correct option

☐	3	
☒	4	
☐	5	
☐	2	

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 03087122922 (Team Hadi Lahore)

Question # 13 of 30 (Start time: 10:31:42 PM, 28 December 2020)

Total Marks:

If the number of samples that are collected is reduced by half, the reconstructed signal will be _____ from/to the original.

Select the correct option

☒	Different	//
☐	Same	//
☐	Equal	//
☐	Opposite	//

MADE BY HADI

Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahor)

Question # 25 of 30 (Start time: 02:56:27 PM, 28 December 2020)

Total Marks: 1

The Binary number 1011.101 has an Integer part represented by _____ and a fraction part _____ separated by a decimal point.

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL: hadirajputofficial@gmail.com
WHATSAPP & CALL: 03087122922

Select the correct option

- | | | |
|----------------------------------|-----------|----|
| ☒ | 1011, 101 | // |
| ☐ | 101, 1011 | // |
| ☐ | 101, 1101 | // |
| ☐ | 10111, 11 | |

MADE BY HADI

Email: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

Question # 20 of 30 (Start time: 10:38:49 PM, 28 December 2020)

Total Marks: 1

_____ Device dissipate varying amount of power depending upon the frequency of operation.

Select the correct option

☐	TTL	//
☒	CMOS	//
☐	Storage	//
☐	Peripheral	//

MADE BY HADIEmail: hadirajputofficial@gmail.com Whatsapp: 0308 7122 922 (Team Hadi Lahore)

HADI VU PAST PAPER

WE DEAL ALL KIND OF VU PROJECT
(PHP, ANDROID, PYTHON)

DEAR STUDENTS

ARE YOU LOOKING
FOR ASSISTANCE

- 1) ASSIGNMENTS
- 2) QUIZZES
- 3) GDB
- 4) GRAND QUIZZES

We Provide, You Solution
of VU Academic Activities
include Assignments,
Quizzes, GDBs, Grand Quizzes
If You Need Help in Services
Kindly inform us.

**TEAM HADI
(VU LAHORE)**



TEAM HADI
(VU LAHORE)



HADI TECH

#PAID_TASK

CONTACT US

CALL & WHATSAPP

0308-7122922