VIRTUAL UNIVERSITY OF PAKISTAN

A Good Education is a Foundation For a Better Future

CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

(Final Term Past Paper)

MADE AND SOLVED BY TEAM HADI

WARNING: Team HADI is not responsible for any mistake or wrong answer. All students reading and using this document may check and confirm the answers at their own.

WhatsApp:03087122922


FACEBOOK ID: https://www.facebook.com/hadipastpapers/

Best of luck!

PAST PAPER

Question No : 1 of 52 Marks: 1 (Budgeted Time 1 Min)

The diagram given below represents _____

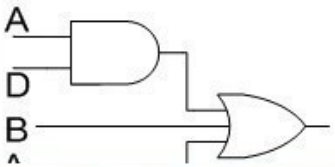

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Demorgans law
- Associative law
- Product of sum form
- Sum of product form

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HAD
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Had

Question No : 2 of 52 Marks: 1 (Budgeted Time 1 Min)

The decimal "8" is represented as _____ using Gray-Code.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 0011
- 1100
- 1000
- 1010

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 3 of 52 Marks: 1 (Budgeted Time 1 Min)

The binary numbers A = 1100 and B = 1001 are applied to the inputs of a comparator. What are the output levels?

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- A > B = 1, A < B = 0, A < B = 1
- A > B = 0, A < B = 1, A = B = 0
- A > B = 1, A < B = 0, A = B = 0
- A > B = 0, A < B = 1, A = B = 1

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 4 of 52 Marks: 1 (Budgeted Time 1 Min)

The simplest of the Encoders are the _____ Encoders

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 2^{n-1}-to-n
- n-to-2n
- 2^n-to-n
- n-to-2^{n-1}

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com

MADE BY HADI

Question No : 5 of 52 Marks: 1 (Budgeted Time 1 Min)

Using multiplexer as parallel to serial converter requires _____ connected to the multiplexer

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- A parallel to serial converter circuit — correct
- A counter circuit
- A BCD to Decimal decoder
- A 2-to-8 bit decoder

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 6 of 52 Marks: 1 (Budgeted Time 1 Min)

74HC163 has two enable input pins which are _____ and _____

-

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- ENP, ENT

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

- ENI, ENC
- ENP, ENC
- ENT, ENI

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 7 of 52 Marks: 1 (Budgeted Time 1 Min)

Given the state diagram of an up/down counter, we can find _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- The next state of a given present state
- The previous state of a given present state
- Both the next and previous states of a given state
- The state diagram shows only the inputs/outputs of a given states

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 8 of 52 Marks: 1 (Budgeted Time 1 Min)

A 4-bit parallel in / serial out shift register contains the value "0100", _____ clock signal(s) will be required to shift the value completely out of the register (i.e. to set the register to 0).

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 1
- 2
- 3
- 4

correct

MADE BY HAD

Question No : 9 of 52 Marks: 1 (Budgeted Time 1 Min)

$(A + B)(A + \overline{B} + C)(\overline{A} + C)$ is an example of _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Product of sum form

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

- Sum of product form
- Demorgans law
- Associative law

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 10 of 52 Marks: 1 (Budgeted Time 1 Min)

The 2's complement method is used to _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Convert binary numbers to decimal
- Convert decimal numbers to binary
- Represent signed numbers

correct

- Represent positive numbers

MADE BY HADI

Question No : 11 of 52 Marks: 1 (Budgeted Time 1 Min)

1011 – 101 = _____

Note: both values are in binary

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 1100
- 0110
- 0011
- 1001

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 12 of 52 Marks: 1 (Budgeted Time 1 Min)

At J = 1, and K = 1, output of JK Flip-flop will be _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Set
- Reset
- Toggle
- Invalid

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 13 of 52 Marks: 1 (Budgeted Time 1 Min)

When one 1 is taken as a group on a Karnaugh map, the number of variables eliminated from the output expression is/are _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 0
- 1
- 2
- 3

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 14 of 52 **Marks: 1 (Budgeted Time 1 Min)**

Using 15 digits (including the sign digit) notation the largest number that can be represented is _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- $999,999,999,999 \times 10^{100}$
- $0.999,999,999,999 \times 10^{100}$
- $999,999,999,999 \times 10^{99}$
- $0.999,999,999,999 \times 10^{99}$ correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lah

Question No : 15 of 52 Marks: 1 (Budgeted Time 1 Min)

The _____ output of first 74HC163 counter is connected to _____ and _____ inputs of other 74HC163 counter to form a single cascaded counter

Answer (Please select your correct option)

- RCO, ENT, ENP
- ENT, RCO, ENP
- ENP, RCO, ENT
- RCO, ENI, ENC

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 16 of 52 Marks: 1 (Budgeted Time 1 Min)

The Sequential circuit whose output depends on the current state and the input is known as _____.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Moore Machine
- Mealy Machine
- Counter
- Flip Flop

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 17 of 52 Marks: 1 (Budgeted Time 1 Min)

The best state assignment tends to _____.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Maximizes the number of state variables that don't change in a group of related states

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HAD
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

- Minimizes the number of state variables that don't change in a group of related states
- Minimizes the equivalent states
- Maximizes the equivalent states

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 18 of 52 Marks: 1 (Budgeted Time 1 Min)

In _____, the $\overline{Q}$ output of the last flip-flop of the shift register is connected to the data input of the first flip-flop.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Moore machine
- Mealy machine
- Johnson counter
- Ring counter

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 19 of 52 Marks: 1 (Budgeted Time 1 Min)

In _____, the Q output of the last flip-flop of the shift register is connected to the data input of the first flip-flop of the shift register.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Moore machine
- Mealy machine
- Johnson counter
- Ring counter

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 20 of 52 Marks: 1 (Budgeted Time 1 Min)

Flip flops are also called _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Bi-stable dualvibrators
- Bi-stable transformer
- Bi-stable multivibrators
- Bi-stable singlevibrators

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

correct

MADE BY HADI

Question No : 21 of 52 Marks: 1 (Budgeted Time 1 Min)

If S=1 and R=0, then Q(t+1) = _____ for positive edge triggered flip-flop

Answer (Please select your correct option)

- 0 correct
- 1
- Invalid
- Input is invalid

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 22 of 52 Marks: 1 (Budgeted Time 1 Min)

The operation of J-K flip-flop is similar to that of the SR flip-flop except that the J-K flip-flop _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Doesn't have an invalid state
- Sets to clear when both J = 0 and K = 0
- It does not show transition on change in pulse
- It does not accept asynchronous inputs

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 23 of 52 Marks: 1 (Budgeted Time 1 Min)

_____ Flip-flops are obsolete now.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Edge-triggered
- Master-Slave

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

- T-Flip-flop
- D-Flip-flop

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 24 of 52 Marks: 1 (Budgeted Time 1 Min)

Bi-stable devices remain in either of their _____ states unless the inputs force the device to switch its state.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Ten
- Eight
- Three
- Two

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 25 of 52 Marks: 1 (Budgeted Time 1 Min)

The counter states can be determined by the formula: _____ ("n" represents the total number of flip-flops).

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- n^2 (n raise to power 2)
- n^2-1 (n raise to power 2 and then minus 1)
- 2^n (2 raise to power n)
- 2^n-1 (2 raise to power n and then minus 1)

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 26 of 52 Marks: 1 (Budgeted Time 1 Min)

RCO Stands for _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Reconfiguration Counter Output
- Reconfiguration Clock Output
- Ripple Counter Output
- Ripple Clock Output

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 27 of 52 Marks: 1 (Budgeted Time 1 Min)

The Sequential circuit, whose output is determined by the current state only is known as _____.

Answer (Please select your correct option)

- Moore Machine — correct
- Mealy Machine
- Counter
- Flip Flop

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL-hadirajputofficial@gmail.com
WHATSAPP& CALL-03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 28 of 52 Marks: 1 (Budgeted Time 1 Min)

A GAL is essentially a _____.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)


- Non-reprogrammable PAL
- PAL that is programmed only by the manufacturer
- Reprogrammable PAL
- Reprogrammable PAL

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

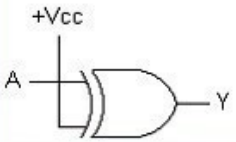Question No : 29 of 52 Marks: 1 (Budgeted Time 1 Min)

The output of this circuit is always _____.



A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 1
- 0
- A
- $\overline{A}$

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 30 of 52 Marks: 1 (Budgeted Time 1 Min)

Which is not characteristic of a shift register?

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Serial in/parallel in
- Serial in/parallel out
- Parallel in/serial out
- Parallel in/parallel out

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 31 of 52 Marks: 1 (Budgeted Time 1 Min)

A Nibble consists of _____ bits

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- 2
- 4 correct
- 8
- 16

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 32 of 52 Marks: 1 (Budgeted Time 1 Min)

Smallest unit of binary data is a _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Bit

correct

- Nibble
- Byte
- Word

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 33 of 52 Marks: 1 (Budgeted Time 1 Min)

The _____ of a ROM is the time it takes for the data to appear at the Data Output of the ROM chip after an address is applied at the address input lines

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Write Time
- Refresh Time
- Refresh Time
- Access Time

correct

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 34 of 52 Marks: 1 (Budgeted Time 1 Min)

In _____, all the columns in the same row are either read or written.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Sequential Access
- MOS Access
- FAST Mode Page Access
- None of given options

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 35 of 52 Marks: 1 (Budgeted Time 1 Min)

FIFO is an acronym for _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- First In, First Out — correct
- Fly in, Fly Out
- Fast in, Fast Out
- None of given options

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 36 of 52 Marks: 1 (Budgeted Time 1 Min)

If the FIFO Memory output is already filled with data then _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- It is locked; no data is allowed to enter
- It is not locked; the new data overwrites the previous data.
- Previous data is swapped out of memory and new data enters
- None of given options

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 37 of 52 Marks: 1 (Budgeted Time 1 Min)

Stack is a _____

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Bust Flash Memory
- FIFO memory
- LIFO memory
- Flash Memory

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 38 of 52 Marks: 1 (Budgeted Time 1 Min)

A flash A/D converter uses :

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Counters

correct not sure

- Flip-flops
- Op-amps
- An integrator

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 39 of 52 Marks: 1 (Budgeted Time 1 Min)

LUT is an acronym for _____

Answer (Please select your correct option)

- Look Up Table

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

- Local User Terminal
- Least Upper Time Period
- None of given options

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 40 of 52 Marks: 1 (Budgeted Time 1 Min)

According to the sampling theorem, the sampling frequency should be :

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please select your correct option)

- Greater than the lowest signal frequency
- Less than half the lowest signal frequency
- Greater than twice the highest signal frequency
- Less than half the highest signal frequency

correct

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI

Question No : 41 of 52 Marks: 2 (Budgeted Time 4 Min)

Divide binary number "1101" by binary number "101", write down all the steps.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:-hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)



Question No : 42 of 52 Marks: 2 (Budgeted Time 4 Min)

Name the single change which can be made to convert a combinational circuit to a sequential circuit?

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)



MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 43 of 52 Marks: 2 (Budgeted Time 4 Min)

Write down the names of two basic operations which are performed on memory?

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 44 of 52 Marks: 2 (Budgeted Time 4 Min)

What is the function of row and column decoders?

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922


Answer (Please click here to Add Answer)

Large memories such as the 16 KB memory have row and column decoders that split the input address into a row address and a column address and activate a row and column select lines respectively.

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

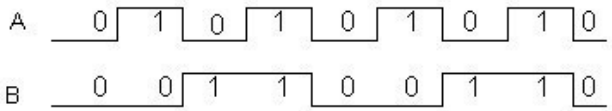Question No : 45 of 52 **Marks: 3 (Budgeted Time 6 Min)**

Following two waves are applied at 2-input AND gate, Draw the output waveform of this gate.




A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

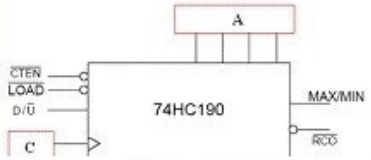Question No : 46 of 52 **Marks: 3 (Budgeted Time 6 Min)**

You are given the block diagram of 74HC190 integrated circuit of 4-bit synchronous up/down counter, Name the pins which are under red boxes.



A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 47 of 52 Marks: 3 (Budgeted Time 6 Min)

Write down three characteristics of serial in / serial out 4-bit left shift register.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL-hadirajputofficial@gmail.com
WHATSAPP& CALL-03087122922

Answer (Please click here to Add Answer)



MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 48 of 52 Marks: 3 (Budgeted Time 6 Min)

Draw the circuit diagram of operational amplifier used as an inverting amplifier.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 49 of 52 Marks: 5 (Budgeted Time 10 Min)

Convert the following Boolean expression into standard SOP form:

$A\bar{B}C + \bar{A}\bar{B} + AB\bar{C}D$

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)

MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)

Question No : 50 of 52 Marks: 5 (Budgeted Time 10 Min)

Draw the next-state table of a 3-bit Up Counter.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)



MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)


Question No : 51 of 52 Marks: 5 (Budgeted Time 10 Min)

Draw a complete test vector table for a 3-bit up/down counter using the following information.

- X is excitation input (if X=0, counter counts upward and vice versa).
- When the Clear input is 0 the output is cleared to 000 irrespective of the X.
- When the Clear input is set to 1 counter functions normally.
- Clear, Clock and X are inputs for up-down counter.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)

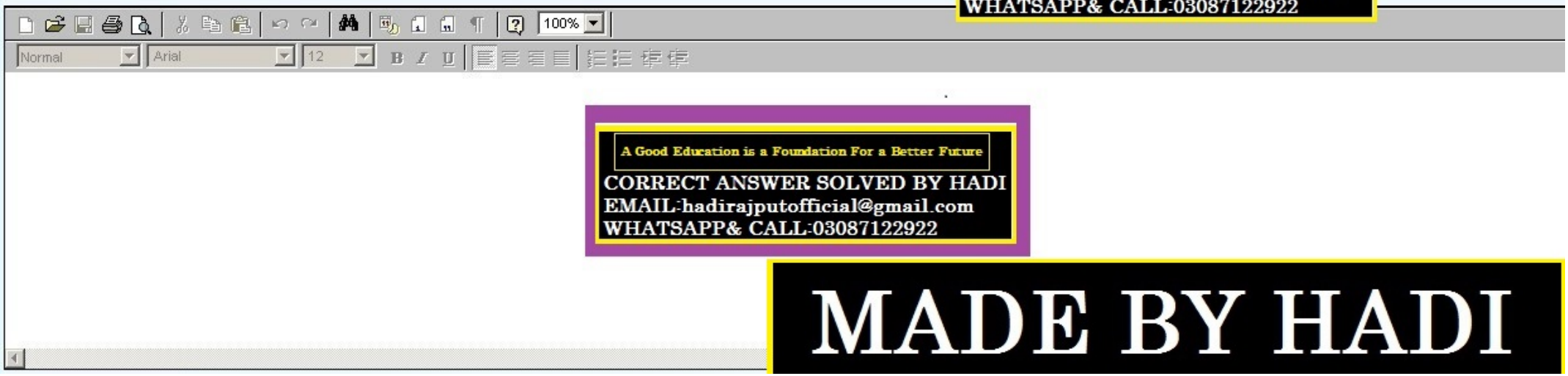

Question No : 52 of 52 Marks: 5 (Budgeted Time 10 Min)

Analog to Digital converters exhibit different types of errors during their conversion operation. Explain at least two.

A Good Education is a Foundation For a Better Future
CORRECT ANSWER SOLVED BY HADI
EMAIL:hadirajputofficial@gmail.com
WHATSAPP& CALL:03087122922

Answer (Please click here to Add Answer)



MADE BY HADI
Email:hadirajputofficial@gmail.comWhatsapp:03087122922(Team Hadi Lahore)