AR Lucky Team

CS302 Quiz No 2





SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(449) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=fd4fc6d1-39fc-4d0e-8305-b165e9a1ad19

Question # 1 of 10 (Start time: 09:44:51 PM, 19 December 2022) **Total Marks:** 1

Addition of two BCD digits requires two ____ Parallel Adder Circuits.

Select the correct option

- 16-bit
- 4-bit

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

- 2-bit
- 8-bit

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:45 AM 12/19/2022

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=d380a7ff-e83d-4145-9bcc-cca1d97d2934

Question # 2 of 10 (Start time: 09:45:48 PM, 19 December 2022) **Total Marks:** 1

+ is written in ABEL as_____ .

Select the correct option

- #

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

- @
- $
- !

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:46 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=52f55eff-2f9f-49b7-ab1a-82ceb08f5305

Restore Down

Question # 3 of 10 (Start time: 09:46:46 PM, 19 December 2022) **Total Marks:** 1

If odd-Parity is being used therefore the 4-bit data and the parity bit should add up to give _____of 1s.

Select the correct option

- Even
- Odd and Prime both
- Prime
- Odd

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:47 AM 12/19/2022

(451) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=0567482d-e21a-45b5-8251-b7bab4ceb813

Error

Question # 4 of 10 (Start time: 09:47:53 PM, 19 December 2022) **Total Marks:** 1

Adjacent 1s detector circuit will have active low output for the input

Select the correct option

- 0110
- 1010
- 1011
- 1101

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:49 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(451) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=9c180d7d-0efc-401a-8fc9-68f1c99525a5

Question # 6 of 10 (Start time: 09:51:07 PM, 19 December 2022) **Total Marks:** 1

A multiplexer circuit has _____ input(s) and _____ output(s).

Select the correct option

- Single, multiple
- Multiple, single
- Multiple, multiple
- Single, single

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:52 AM 12/19/2022

(451) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=78eb1f91-1fb1-4a3d-bd47-8112f6a33130

Question # 7 of 10 (Start time: 09:52:50 PM, 19 December 2022) **Total Marks:** 1

Why demultiplexer is called a data distributor?

Select the correct option

- The output will be distributed to one of the inputs
- One of the inputs will be selected for the output
- The input will be distributed to one of the outputs
- Single input to Single Output

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:55 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(452) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=5caada6a-4c00-4352-a8eb-aecc9e3fec25

Question # 9 of 10 (Start time: 09:57:12 PM, 19 December 2022) **Total Marks:** 1

In a Digital System, Binary data is used and represented in_____.

Select the correct option

- Serial
- Static
- Variable
- Parallel

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:58 AM 12/19/2022

(452) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=43e83a97-878f-4e94-9388-5d858b831520

Question # 10 of 10 (Start time: 09:58:25 PM, 19 December 2022) **Total Marks:** 1

How many of enable inputs is(are) active-low in 74XX138 3-to-8 Decoder?

Select the correct option

- Four
- One
- Three
- Two

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 8:59 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=96fb7c81-e19b-4473-8236-6c7f3f0f11e9

Question # 1 of 10 (Start time: 10:02:14 PM, 19 December 2022) **Total Marks:** 1

Which of the following is the MSI version of the Look-Ahead Carry Generator, which provides identical inputs and outputs except for the C4 output?

Select the correct option

- 74XX180
- 74XX181
- 74XX182 — Correct Answer
  Email : abdulrehmanvu7@gmail.com
  Phone No : 03042387216
- 74XX183

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 9:03 AM 12/19/2022

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=d5ecc9d0-1586-49ec-8527-4e3011e72646

Question # 2 of 10 (Start time: 10:03:45 PM, 19 December 2022) **Total Marks:** 1

In 8-input multiplexer, when ___ is set to 0, the first multiplexer is selected allowing its inputs 1C0, 1C1, 1C2 and 1C3 to be selected.

Select the correct option

- B
- A
- D
- C — Correct Answer
  Email : abdulrehmanvu7@gmail.com
  Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 9:04 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=44a9a079-aec3-4ce0-8e82-6a9f98732430

Restore Down

Error

Question # 3 of 10 (Start time: 10:04:46 PM, 19 December 2022) **Total Marks:** 1

A circuit that converts the n inputs to 2^n outputs is called_____.

Select the correct option

- Encoder
- Shifter
- Comparator
- Decoder

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search

15°C Clear 9:05 AM 12/19/2022

(452) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=a50220ed-b4c9-420e-aedd-ddf23c958de9

Error

Question # 4 of 10 (Start time: 10:05:35 PM, 19 December 2022) **Total Marks:** 1

In K-map simplification method, a group of four adjacent 1's lead to a term with_____

Select the correct option

- Two literals less than the total number of variables

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

- Three literals less than the total number of variables
- Four literals less than the total number of variables
- One literal less than the total number of variables

Click to Save Answer & Move to Next Question

Type here to search

15°C Clear 9:07 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(452) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=64836498-7353-4d93-a5c4-5c8b0e328a3b

Question # 5 of 10 (Start time: 10:07:12 PM, 19 December 2022) **Total Marks:** 1

In 16-bit ALU, the G output is activated if the 4-bit unit generates a _____ irrespective of _____.

Select the correct option

- Carry in, carry out
- Carry in, input number
- Input number, carry in
- Carry out, carry in

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 9:08 AM 12/19/2022

(452) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=38891e16-6050-441d-b7b4-74e9f4e79aff

Question # 6 of 10 (Start time: 10:08:23 PM, 19 December 2022) **Total Marks:** 1

In 1-to-4 demultiplexer, how many select lines are required

Select the correct option

- 2

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216


- 5
- 3
- 4

Click to Save Answer & Move to Next Question

Type here to search | 15°C Clear | 9:09 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

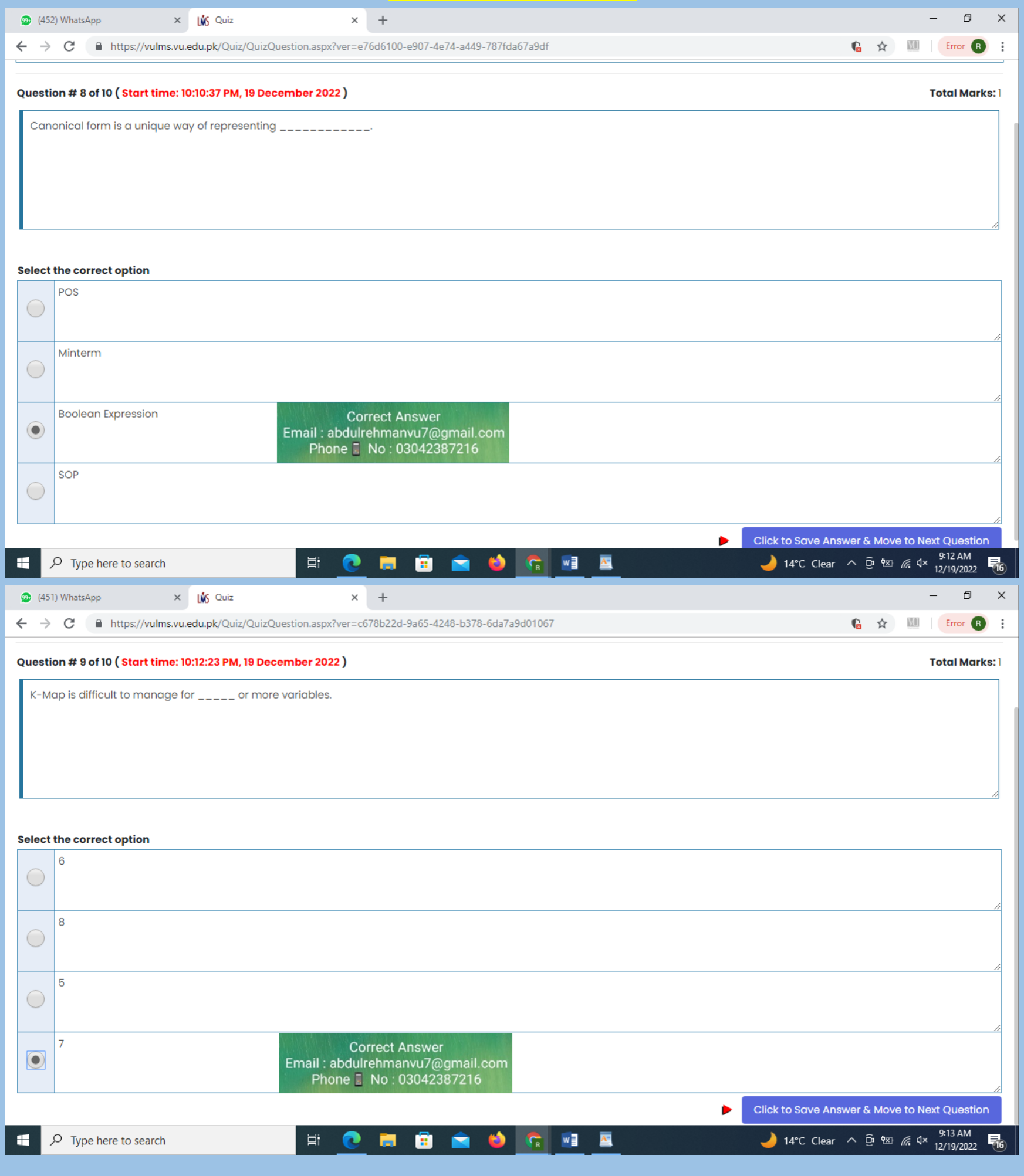

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(451) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=123f89f7-ba00-4cd0-82ad-d0e469f56f5c

Question # 10 of 10 (Start time: 10:13:38 PM, 19 December 2022) **Total Marks:** 1

_____ is used when the output is connected back to the input of the PAL or if the output pin is used as an input only.

Select the correct option

- Programmable polarity
- Combinational Output
- Combinational Input/Output

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

- Combinational Input

Click to Save Answer & Move to Next Question

Type here to search | 14°C Clear | 9:14 AM 12/19/2022

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=7c7db292-0e78-4881-81f0-98b1b727e35d

Question # 1 of 10 (Start time: 12:12:12 AM, 20 December 2022) **Total Marks:** 1

In 8-input multiplexer, when ___ is set to 0, the first multiplexer is selected allowing its inputs 1C0, 1C1, 1C2 and 1C3 to be selected.

Select the correct option

- A
- B
- D
- C

Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216

Click to Save Answer & Move to Next Question

Type here to search | 13°C Clear | 11:13 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

(450) WhatsApp | Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=c54421ae-ff25-431b-a0a6-d8e64101c8c3

Question # 2 of 10 (Start time: 12:13:43 AM, 20 December 2022) **Total Marks:** 1

How many outputs can an integrated circuit comparator have?

Select the correct option

- (●) Three — Correct Answer
  Email : abdulrehmanvu7@gmail.com
  Phone No : 03042387216
- ( ) One
- ( ) Two
- ( ) Four

Click to Save Answer & Move to Next Question

Type here to search | 13°C Clear | 11:15 AM 12/19/2022

Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=3da590b4-69ba-428e-b8db-5a72a67ec69d

Question # 4 of 10 (Start time: 12:17:19 AM, 20 December 2022) **Total Marks:** 1

The Quine-McCluskey method has _____ number of steps.

Select the correct option


- ( ) 5
- ( ) 4
- (●) 2 — Correct Answer
  Email : abdulrehmanvu7@gmail.com
  Phone No : 03042387216
- ( ) 3

Click to Save Answer & Move to Next Question

Type here to search | 13°C Clear | 11:18 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

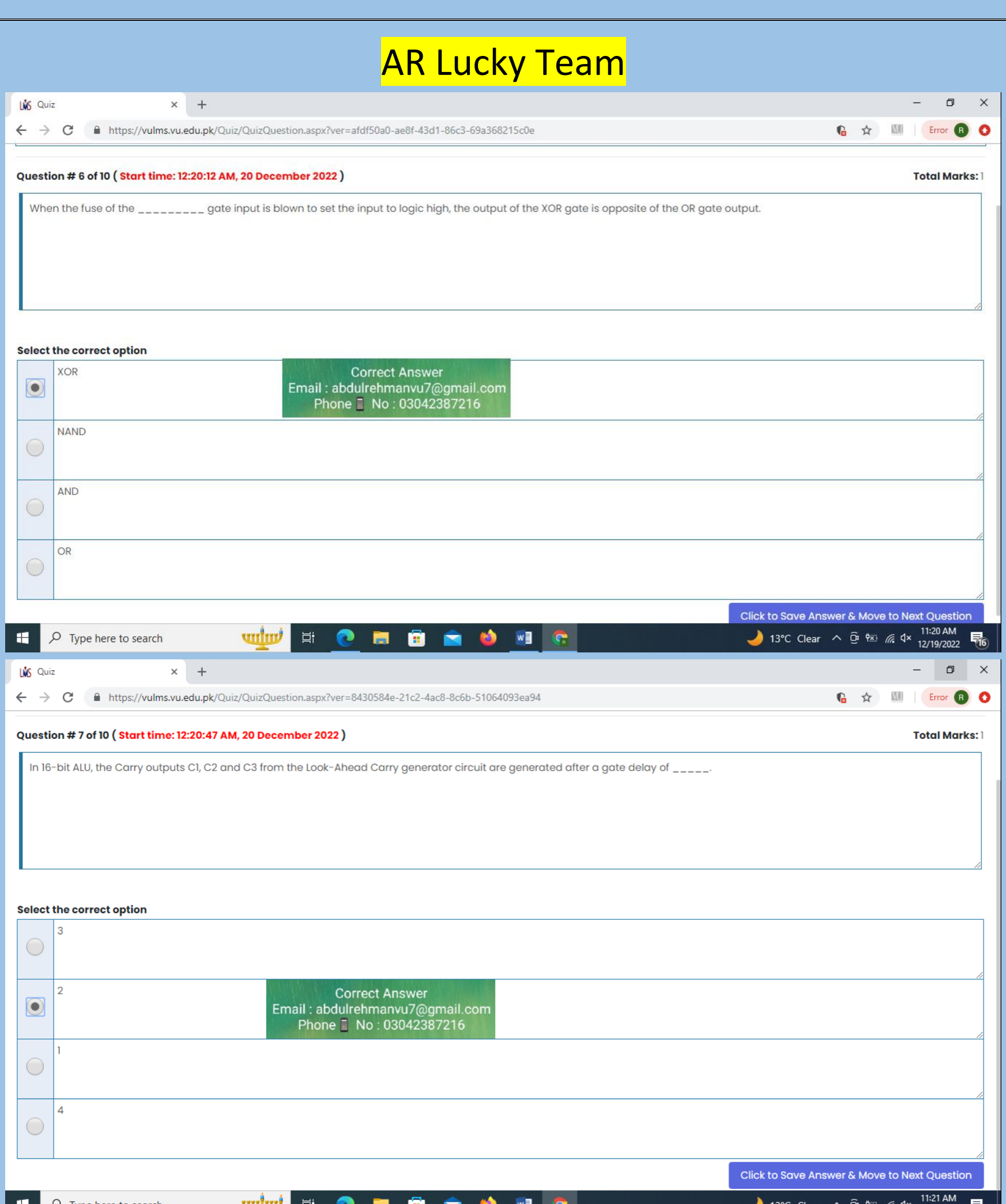

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=96f9aab5-238c-414b-88f9-2c1cbeb6b48f

Error

Question # 8 of 10 (Start time: 12:21:22 AM, 20 December 2022) **Total Marks:** 1

How many data select lines are required for selecting eight inputs?

Select the correct option

- [x] 3 — Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216
- [ ] 1
- [ ] 2
- [ ] 4

Click to Save Answer & Move to Next Question

Type here to search

13°C Clear 11:21 AM 12/19/2022

Quiz

https://vulms.vu.edu.pk/Quiz/QuizQuestion.aspx?ver=16741bbd-8966-4488-b962-10d67e81c830

Error

Question # 9 of 10 (Start time: 12:22:10 AM, 20 December 2022) **Total Marks:** 1

In Cascading Priority Encoders, the EO output is connected to the EI input of the encoder which handles _____.

Select the correct option

- [x] Lower priority inputs — Correct Answer
Email : abdulrehmanvu7@gmail.com
Phone No : 03042387216
- [ ] Lower priority outputs
- [ ] Higher priority inputs
- [ ] Higher priority outputs


Click to Save Answer & Move to Next Question


Type here to search

13°C Clear 11:22 AM 12/19/2022

SUBSCRIBE AR Lucky Bahi

AR Lucky Team

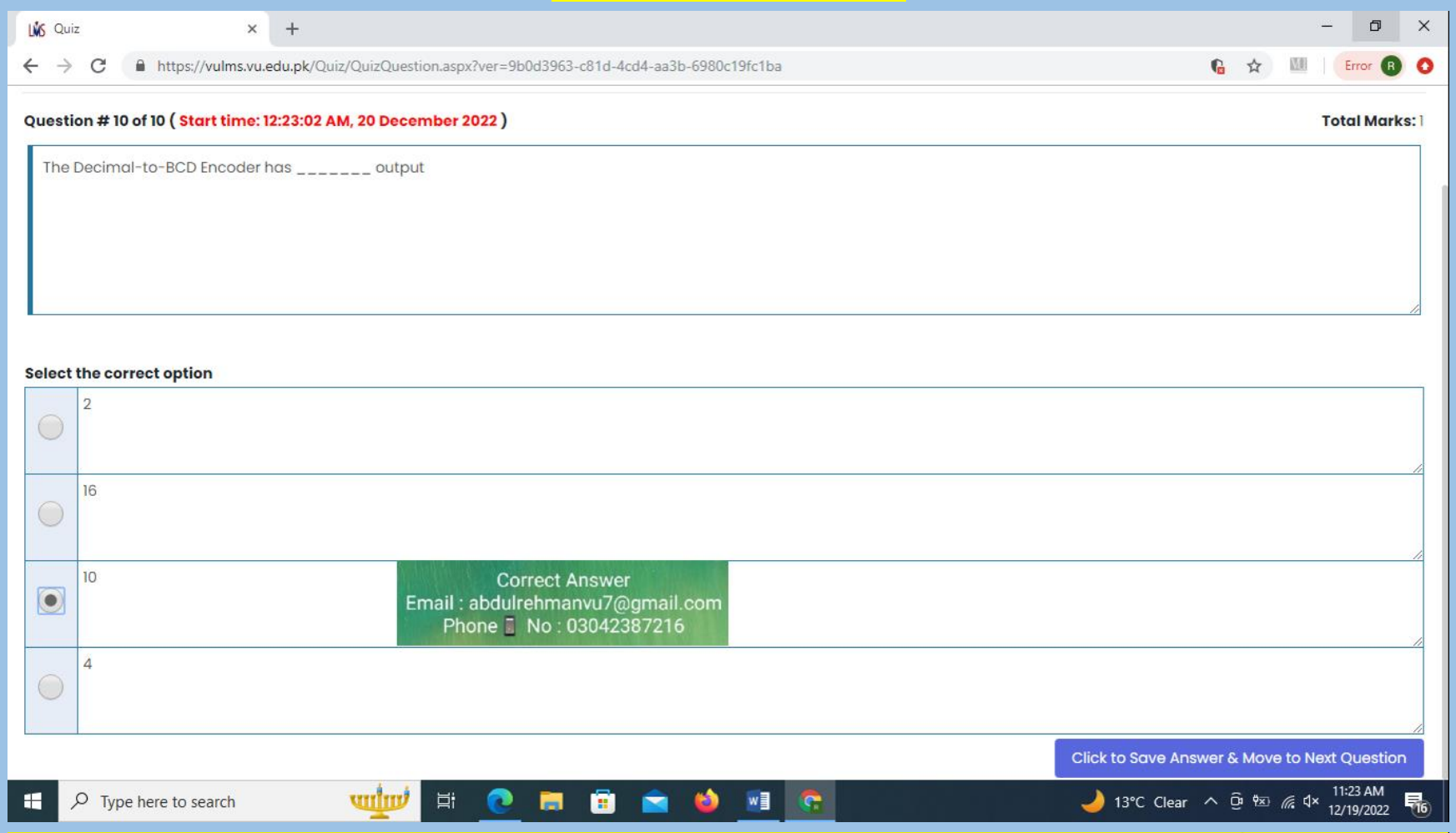

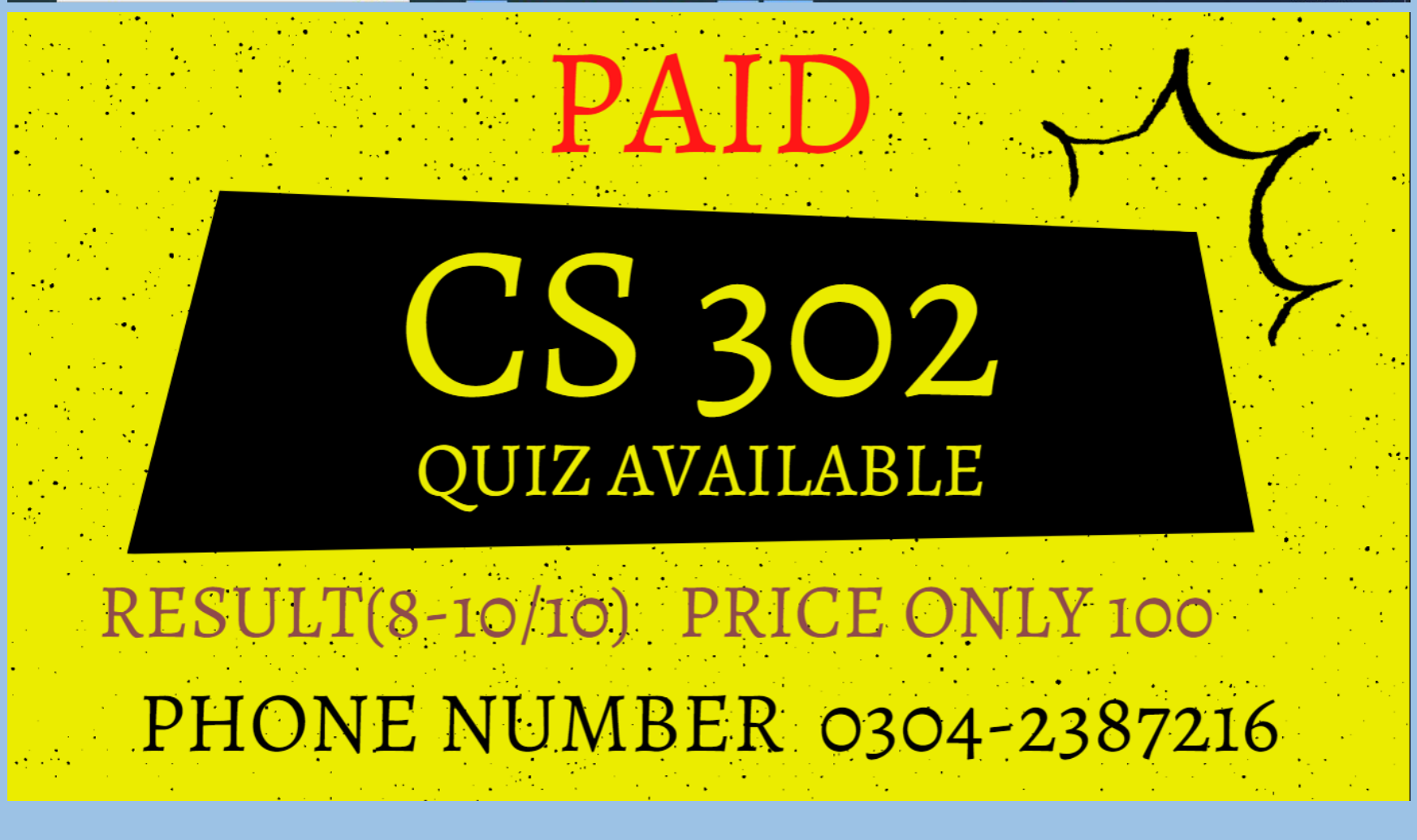



AR Lucky Team

