
QUIZ#2
CS302P
FALL-2024
BY
BUTTERCUP
FOR LMS HANDLING
CONTACT
0324-9427076

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Question # 4 of 5 (Start time: 10:38:55 PM, 15 November 2024)

To draw a logic circuit for boolean expression **AB'+C**, how many gates are used?

Select the correct option

○	2
◉	3
○	4
○	1

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November 202

Question # 5 of 5 (Start time: 10:39:42 PM, 15 November 2024)

Total Marks

_____ gate with a bubble at the output is know as NOR gate.

Select the correct option

Reload Math Equations

- ○ AND
- ◉ NAND
- ○ NOT
- ○ OR

Click to Save Answer & Move to Next Question

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November

Question # 3 of 5 (Start time: 10:38:04 PM, 15 November 2024)

Total M

DE Morgan's Theory is used to convert _____ gates to _____ones.

Select the correct option

Reload Math Equati

○	AND/XOR, XOR/AND
○	AND/OR, NOR/NAND
◉	AND/NAND, OR/NOR
○	OR/NOT, NOT/OR

Click to Save Answer & Move to Next Questi

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November 2024

Question # 2 of 5 (Start time: 10:37:25 PM, 15 November 2024) **Total Marks:** 1

_____ gate with a bubble at the output is know as NAND gate.

Select the correct option

Reload Math Equations

- (●) NOT
- ( ) OR
- ( ) NOR
- ( ) AND

Click to Save Answer & Move to Next Question

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November 2024

Question # 1 of 5 (Start time: 10:36:16 PM, 15 November 2024) **Total Marks:** 1

According to De-Morgan's law, which of the following is **TRUE**?

Select the correct option

Reload Math Equations

- (●) $A + B = (A'. B')'$
- ( ) $A . B = (A'. B')'$
- ( ) $A+B = (A+B)'$
- ( ) $(A + B)' = (A' + B')'$

Click to Save Answer & Move to Next Question

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 2 - (Not Graded))

Qui

Question # 3 of 5 (Start time: 04:06:07 PM, 08 November 2024)

According to the distributive law of Boolean algebra, which of the following statements is **TRUE**?

Select the correct option

○	$X + (Y\ Z) = XYZ$
○	$X + (Y\ Z) = (X + Y)\ (X + Z)$
○	$X + (Y\ Z) = XY+XZ$
●	$X + (Y\ Z) = X+Y+Z$

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 2 - (Not Graded))

Quiz Start Time:

Question # 2 of 5 (Start time: 04:05:23 PM, 08 November 2024)

A logic circuit having two inputs A and B can have _____ different input combinations.

Select the correct option

○	1
●	4
○	3
○	2

Click to Save Answ

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 2 - (Not Graded))

Qu

Question # 1 of 5 (Start time: 04:04:31 PM, 08 November 2024)

According to the laws of boolean algebra, the expression **A(A' + B)** is equivalent to _____

Select the correct option

○	A + A' + B
○	A'B
○	AA'B
◉	AB

Click

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 2 - (Not Graded))

Qui

Question # 3 of 5 (Start time: 04:06:07 PM, 08 November 2024)

According to the distributive law of Boolean algebra, which of the following statements is **TRUE**?

Select the correct option

○	X + (Y Z) = XYZ
◉	X + (Y Z) = (X + Y) (X + Z)
○	X + (Y Z) = XY+XZ
○	X + (Y Z) = X+Y+Z

Click t

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 2 - (Not Graded))

Qu

Question # 4 of 5 (Start time: 04:07:41 PM, 08 November 2024)

According to the commutative law of Boolean algebra, which of the following expression is **TRUE**?

Select the correct option

○	A.B = A+B
●	A.B = B.A
○	A.B' = A'.B
○	A'.B' = A.B

Click

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 2 - (Not Graded))

Quiz Start Time: 04:04 PM, 08 November 2024

Question # 5 of 5 (Start time: 04:09:22 PM, 08 November 2024) **Total Marks:** 1

If **Z = A' + B + C' + D** then what should be the values of A, B, C, and D so that the expression returns **Z = 0.**

Select the correct option

Reload Math Equations

◉	A = 0, B = 1, C = 0, D = 0
○	A = 1, B = 0, C = 0, D = 0
○	A = 1, B = 0, C = 1, D = 0
○	A = 1, B = 0, C = 1, D = 1

Click to Save Answer & Move to Next Question

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November 2024

Question # 1 of 5 (Start time: 10:36:16 PM, 15 November 2024) **Total Marks:** 1

According to De-Morgan's law, which of the following is **TRUE**?

Select the correct option

Reload Math Equations

◉	$A + B = (A'.B')'$
○	$A . B = (A'.B')'$
○	$A+B = (A+B)'$
○	$(A + B)' = (A' + B')'$

Click to Save Answer & Move to Next Question

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November 2024

Question # 2 of 5 (Start time: 10:37:25 PM, 15 November 2024) **Total Marks:** 1

_____ gate with a bubble at the output is know as NAND gate.

Select the correct option

Reload Math Equations

◉	NOT
○	OR
○	NOR
○	AND

Click to Save Answer & Move to Next Question

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November

Question # 3 of 5 (Start time: 10:38:04 PM, 15 November 2024)

Total M

DE Morgan's Theory is used to convert _____ gates to _____ones.

Select the correct option

Reload Math Equati

- AND/XOR, XOR/AND
- AND/OR, NOR/NAND
- AND/NAND, OR/NOR
- OR/NOT, NOT/OR

Click to Save Answer & Move to Next Questi

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Question # 4 of 5 (Start time: 10:38:55 PM, 15 November 2024)

To draw a logic circuit for boolean expression **AB'+C**, how many gates are used?

Select the correct option

○	2
◉	3
○	4
○	1

CS302P - Digital Logic Design (Practical) (Attendance Quiz # 3 - (Not Graded))

Quiz Start Time: 10:36 PM, 15 November 202

Question # 5 of 5 (Start time: 10:39:42 PM, 15 November 2024)

Total Marks

_____ gate with a bubble at the output is know as NOR gate.

Select the correct option

Reload Math Equations

- ○ AND
- ◉ NAND
- ○ NOT
- ○ OR

Click to Save Answer & Move to Next Question


QUIZ#2
CS302P
FALL-2024
BY
BUTTERCUP
FOR LMS HANDLING
CONTACT
0324-9427076