PAID ASSIGNEMNTS QUIZES GDB CONTACT 03147094561

CS302P QUIZ#4



SUBSCRIBE MY YOUTUBE CHANNEL

Study With Hamza 25

https://www.youtube.com/@studywithhamza25

PAID ASSIGNEMNTS QUIZES GDB CONTACT 03147094561

1. When implementing a half adder by using gates, which of the following gates is used to return carry bit as an output?

   a. AND
   b. XOR
   c. NAND
   d. OR *

2. What is the maximum possible range of bit-count specifically in n-bit binary counter consisting of 'n' number of flip-flops?

   a. 0 to $2^n - 1$ *
   b. 0 to $2^n + 1$
   c. 0 to 2^{n+1}
   d. 0 to 2^n

3. Which of the following is the modified code of Excess-3 code?

   a. EBDIC
   b. BCD
   c. Gray Code
   d. ASCII

4. There are _____ cells in a 4-variable K-map.

   a. 24
   b. 20
   c. 8
   d. 16

@hamzabahtti25

PAID ASSIGNEMNTS QUIZES GDB CONTACT 03147094561

5. It should be kept in mind that don't care terms should be used along with the terms that are present in _____.
   a. Expressions
   b. Latches
   c. K-Map
   d. Minterms
6. In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the mutiplexer?
   a. Vcc
   b. G'
   c. Y
   d. W
7. A half adder can be built by using the combination of _____ and _____ gates.
   a. AND, XOR
   b. OR, XOR
   c. AND, NOT
   d. AND, OR
8. In a full adder circuit having inputs **A = 1, B =1, Cin = 0**, the outputs **S** and **Cout** will be _____.
   a. S = 1, Cout = 1
   b. S = 0, Cout = 1
   c. S = 0, Cout = 0

PAID ASSIGNEMNTS QUIZES GDB CONTACT 03147094561

d. S = 1, Cout = 0

9. There are _____ cells in a 5-variable K-map
   a. 16
   b. 64
   c. 32
   d. 24

10. Which of the following symbols is used to represent XOR operation?
   a. ^
   b. +
   c. ⊕
   d. x

SUBSCRIBE MY YOUTUBE CHANNEL
JOIN OUR WHATSAPP GROUPS & CHANNEL
FOR LATEST SOLUTION'S
https://www.youtube.com/@studywithhamza25

WHATSAPP GROUP 1
JOIN NOW
WHATSAPP GROUP2
JOIN NOW
Join WHATSAPP CHANNEL
JOIN NOW