VU Quiz Collection

Total Quizzes: 10

Courses: CS302

Generated: 12/30/2025, 9:05:35 PM

Powered by Firewall Bypass VU Extension
Waseem Akram | wasii.dev | +1 (226) 798-2360

VU Quiz Collection

Generated by Firewall Bypass VU Extension

Quiz 1 - CS302

Question:

In case of cascading Integrated Circuit counters, the enable inputs and RCOof the Integrated Circuit counters allow cascading of multiple counters together

Options:

A. True

B. False

Copied: 12/30/2025, 9:02:37 PM

Quiz 2 - CS302

Question:

A one-shot mono-stable device contains _____

Options:

A. NOR gate, Resistor, Capacitor and NOT Gate

B. NAND gate, Resistor, Capacitor and NOT Gate

C. AND gate, Resistor, Capacitor and NOT Gate

D. XNOR gate, Resistor, Capacitor and NOT Gate

Copied: 12/30/2025, 9:02:52 PM

Quiz 3 - CS302

Question:

The GAL22V10 is a popular GAL device having _____ inputs and ten inputs/outputs.

Options:

A. 20

B. 12

C. 10

D. 22

Copied: 12/30/2025, 9:03:12 PM

Quiz 4 - CS302

Question:

Demultiplexer is also called _____

Options:

A. Data encoder

B. Data distributor

C. Data router

D. Data selector

Copied: 12/30/2025, 9:03:32 PM

Quiz 5 - CS302

Question:

PLDs have In-System Programming (ISP) capability that allows the _____ to be programmed after they have been installed on a circuit board.

Options:

A. EPROM

B. PLAs

C. PALs

D. PLDs

Copied: 12/30/2025, 9:03:48 PM

Quiz 6 - CS302

Question:

A _____ output can change from one state to the other by applying appropriate inputs.

Options:

A. system

B. counter

C. latch

D. flip flop

Copied: 12/30/2025, 9:04:03 PM

Quiz 7 - CS302

Question:

Two 2-input, 4-bit multiplexers 74X157 can be connected to implement a ____ multiplexer.

Options:

A. 2-input, 4-bit

B. 4-input, 16-bit

C. 4-input, 8-bit

D. 2-input, 8-bit

Copied: 12/30/2025, 9:04:18 PM

Quiz 8 - CS302

Question:

The 74HC163 is a 4-bit Synchronous Counter.it has.....data output pins

Options:

A. 4

B. 2

C. 8

D. 6

Copied: 12/30/2025, 9:04:41 PM

Quiz 9 - CS302

Question:

In 8-input multiplexer, the two outputs are connected through a/an _____ gate.

Options:

A. NOT

B. OR

C. AND

D. NOR

Copied: 12/30/2025, 9:05:02 PM

Quiz 10 - CS302

Question:

In asynchronous digital systems all the circuits change their state with respect to a common clock

Options:

A. True

B. False

Copied: 12/30/2025, 9:05:23 PM