VU Quiz Collection

Total Questions: 10 from 10 Quiz(es)

Courses: CS302

Generated: 1/8/2026, 10:17:35 PM

Powered by Firewall Bypass VU Extension
Waseem Akram | wasii.dev | +1 (226) 798-2360

Quiz 1 - CS302 (Q1/10)

Question:

With a 100 KHz clock frequency, eight bits can be serially entered into a shift register in

Options:

A. 10 micro seconds

B. 8 micro seconds

C. 80 micro seconds

D. 80 mili seconds

Copied: 1/8/2026, 10:11:10 PM

Quiz 2 - CS302 (Q2/10)

Question:

When an eight bit serial in/out shift register is used for a 24 micro seconds time delay, the clock frequency must be

Options:

A. 41.67 KHz

B. 125 KHz

C. 8 MHz

D. 333 KHz

Copied: 1/8/2026, 10:12:02 PM

Quiz 3 - CS302 (Q3/10)

Question:

According to Moore circuit, the output of synchronous sequential circuit depend/s on _____ of flip flop.

Options:

A. Next State

B. External Inputs

C. Present State

D. Previous State

Copied: 1/8/2026, 10:12:52 PM

Quiz 4 - CS302 (Q4/10)

Question:

Once the state diagram is drawn for any sequential circuit the next step is to draw

Options:

A. Transiation table

B. Next-state table

C. Logic expression

D. Karnaugh map

Copied: 1/8/2026, 10:13:49 PM

Quiz 5 - CS302 (Q5/10)

Question:

Which mechanism allocate the binary values to the states in order to reduce the cost of the combinational circuits?

Options:

A. State Evaluation

B. State Minimization

C. State Assignment

D. State Reduction

Copied: 1/8/2026, 10:14:11 PM

Quiz 6 - CS302 (Q6/10)

Question:

The normal data inputs to a flip-flop (D, S and R, J and K, T) are referred to as _____ inputs.

Options:

A. Synchronous

B. Asynchronous

C. Sequential

D. Combinational

Copied: 1/8/2026, 10:14:44 PM

Quiz 7 - CS302 (Q7/10)

Question:

If data is brought into the J terminal and its complement to the K terminal, a J-K flip-flop operates as a(n) _____.

Options:

A. S-C flip-flop

B. D flip-flop

C. S-R flip-flop

D. N flip-flop

Copied: 1/8/2026, 10:15:13 PM

Quiz 8 - CS302 (Q8/10)

Question:

Karnaugh map is used in designing

Options:

A. a clock

B. All of the above

C. a counter

D. an UP/DOWN counter

Copied: 1/8/2026, 10:16:19 PM

Quiz 9 - CS302 (Q9/10)

Question:

The 3-bit up counter can be implemented using _____ flip-flop(s).

Options:

A. S-R Flip-flips and D-Flip-flops

B. S-R Flip-flops Only

C. D-Flip-flop Only

D. S-R Flip-flops or D-Flip-flops

Copied: 1/8/2026, 10:17:07 PM

Quiz 10 - CS302 (Q10/10)

Question:

In the keyboard encoder, how many times per second does the ring counter scan the key board?

Options:

A. 600 scans/second

B. 625 scans/second

C. 650 scans/second

D. 700 scans/second

Copied: 1/8/2026, 10:17:22 PM