VU Quiz Collection

Total Quizzes: 10

Courses: CS420 - Web Development for Portable Devices (Quiz#2), CS302 - Digital Logic Design (Semester Quiz # 0

Generated: 11/25/2025, 11:10:47 AM

Powered by Firewall Bypass VU Extension
Waseem Akram | wasii.dev | 03137119351

Quiz 1 - CS420 - Web Development for Portable Devices (Quiz#2)

Question:

By default, the background-image property repeats an image _____.

Options:

A. Both horizontally and vertically

B. None of the given

C. Horizontally

D. Vertically

Copied: 11/25/2025, 11:04:43 AM

Quiz 2 - CS420 - Web Development for Portable Devices (Quiz#2)

Question:

If the transparent part of the image has rounded or diagonal edges, which format is suitable?

Options:

A. Transparent GIF

B. GIF

C. PNG

D. JPG

Copied: 11/25/2025, 11:04:56 AM

Quiz 3 - CS420 - Web Development for Portable Devices (Quiz#2)

Question:

Physical pixel size of IPhone 6 Plus is _____ pixels.

Options:

A. 720*340

B. 840*440

C. 1080*1920

D. 1020*240

Copied: 11/25/2025, 11:05:11 AM

Quiz 4 - CS420 - Web Development for Portable Devices (Quiz#2)

Question:

The bulk of _____ work is done through .htaccess and PHP 5.x, which offers a great solution without complete dependency on JavaScript.

Options:

A. Responsive images

B. Adaptive images

C. Fixed images

D. Fluid images

Copied: 11/25/2025, 11:05:24 AM

Quiz 5 - CS302 - Digital Logic Design (Semester Quiz # 02)

Question:

The limitation in implementation of parallel binary adders is known as _____.

Options:

A. Carry propagation.

B. Delay.

C. Carry input.

D. Carry output.

Copied: 11/25/2025, 11:08:04 AM

Quiz 6 - CS302 - Digital Logic Design (Semester Quiz # 02)

Question:

In look ahead circuits G stands for_____.

Options:

A. Carry propagate.

B. Propagation delay.

C. Carry input.

D. Carry generate.

Copied: 11/25/2025, 11:08:41 AM

Quiz 7 - CS302 - Digital Logic Design (Semester Quiz # 02)

Question:

Which of the following expression is in the product-of-sums form?

Options:

A. (A + B)(C + D)

B. AB + CD

C. AB(CD)

D. (AB)(CD)

Copied: 11/25/2025, 11:09:07 AM

Quiz 8 - CS302 - Digital Logic Design (Semester Quiz # 02)

Question:

For a Standard SOP expression, a _____ is placed in the cell corresponding to the product term (Minterm) present in the expression.

Options:

A. 0

B. 1

C. X (don’t care condition)

D. Any of given option depending on SOP term.

Copied: 11/25/2025, 11:10:00 AM

Quiz 9 - CS302 - Digital Logic Design (Semester Quiz # 02)

Question:

Which of the following is the MSI version of the Look-Ahead Carry Generator, which provides identical inputs and outputs except for the C4 output?

Options:

A. 74XX180

B. 74XX181

C. 74XX183

D. 74XX182

Copied: 11/25/2025, 11:10:19 AM

Quiz 10 - CS302 - Digital Logic Design (Semester Quiz # 02)

Question:

Implementing the Adjacent 1s detector circuit directly from the function table based on the SOP form requires _____ gates for the 8 product terms (minterms) with an 8-input OR gate.

Options:

A. 8 NOR

B. 8 AND

C. 8 XOR

D. 8 OR

Copied: 11/25/2025, 11:10:46 AM