CS302P - Quiz No.04

Date: 08 January 2026

Q.1 In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the mutiplexer?

A. Y

B. W

C. G'

D. Vcc

Q.2 Which of the following gates is used for parity generation for a binary data string?


A. XOR

B. NOR

C. OR

D. AND

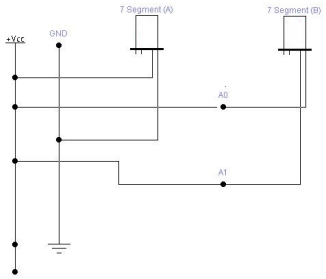Q.3 Consider the below given EWB circuit, what values will be displayed on 7-segment displays A and B when the circuit simulation is activated in EWB?



A. 0, 1

B. 1, 3

C. 2, 3

D. 3, 3

Q.4 A full adder circuit takes _____ bit(s) as input and returns _____ bit(s) as output.

A. 3, 2

B. 2, 1

C. 3, 1

D. 2, 2

Q.5 Which of the following symbols is used to represent XOR operation?

A. ⊕

B. +

C. x

D. ^

Q.6 How many select lines would be required for an 8x1 multiplexer?

A. 1
B. 8
C. 3
D. 2

Q.7 To create a Johnson Counter by using D-flip flops, how flip flops should be connected together?

A. Q' output of previous flip flop should be connected to D input of second flip flop
B. Q output of previous flip flop should be connected to D input of second flip flop
C. Q output of previous flip flop should be connected to clock input of second flip flop
D. Q' output of previous flip flop should be connected to clock input of second flip flop

---

Q.8 Reflected Binary Code is also known as _____ code.

A. Excess-3
B. ASCII
C. Gray Code
D. BCD

Q.9 Which of the following is an invalid BCD code?

A. 0101
B. 1001
C. 0011
D. 1101

Q.10 Convert the Gray code 1011 to binary.

A. 1011
B. 0111
C. 1010
D. 1101
