CS302P - Quiz No.04

Date: 08 January 2026

Q.1 Reflected Binary Code is also known as _____ code.

A. BCD

B. ASCII

C. Gray Code

D. Excess-3

Q.2 To create a Johnson Counter by using D-flip flops, how flip flops should be connected together?

A. Q' output of previous flip flop should be connected to D input of second flip flop

B. Q' output of previous flip flop should be connected to clock input of second flip flop

C. Q output of previous flip flop should be connected to D input of second flip flop

D. Q output of previous flip flop should be connected to clock input of second flip flop

---

Q.3 Total number of inputs in a half adder is _____.

A. 3

B. 2

C. 4

D. 1

Q.4 Which of the following gates is used for parity generation for a binary data string?

A. XOR

B. AND

C. NOR

D. OR

Q.5 A decimal counter has _____ states.

A. 2

B. 10

C. 7

D. 9

Q.6 In a full adder circuit having inputs A = 1, B =1, Cin = 0, the outputs S and Cout will be _____.

A. S = 1, Cout = 0

B. S = 1, Cout = 1

C. S = 0, Cout = 1

D. S = 0, Cout = 0

Q.7 Following diagram is of _____ code conversion.
https://storage.googleapis.com/tb-img/production/20/09/F1_S.B_Deepak_03.03.2020_D%201.png

A. ASCII

B. Gray

C. BCD

D. Excess-3

Q.8 When implementing a half adder by using gates, which of the following gates is used to return carry bit as an output?

A. AND

B. XOR

C. NAND

D. OR

Q.9 To build a full adder using gates, how many gates are required?


A. 2 AND gates, 3 OR gates, 1 XOR gates

B. 2 AND gates, 2 OR gates, 2 XOR gates

C. 1 AND gate, 2 OR gates, 1 XOR gate

D. 2 AND gates, 2 XOR gates, 1 OR gate

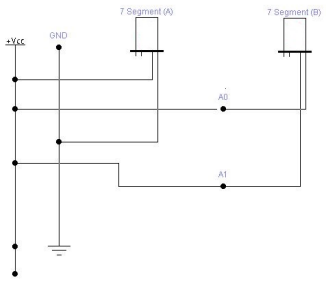Q.10 Consider the below given EWB circuit, what values will be displayed on 7-segment displays A and B when the circuit simulation is activated in EWB?



A. 3, 3

B. 2, 3

C. 0, 1

D. 1, 3
