1. To build a full adder using gates, how many gates are required?

A. 1 AND gate, 2 OR gates, 1 XOR gate
B. 2 AND gates, 3 OR gates, 1 XOR gates
C. 2 AND gates, 2 XOR gates, 1 OR gate
D. 2 AND gates, 2 OR gates, 2 XOR gates

---

2. Which of the following symbols is used to represent XOR operation?

A . "•
B. +
C. x
D. ^

---

3. _____ gate with a bubble at the output is know as NAND gate

A. NOT
B. OR
C. AND
D. NOR

---

4. It should be kept in mind that don't care terms should be used along with the terms that are present in _____

A. Latches
B. Minterms
C. Expressions
D. K-Map

---

5. A Karnaugh map (K-map) is an abstract form of _____ diagram organized as a matrix of squares

A. Cycle Diagram
B. Triangular Diagram
C. Venn Diagram
D. Block diagram

VU TOOLKIT BY PARADOXCIAL