CS302P - Quiz No.8

Date: 02 January 2026

Q.1 Total number of inputs in a half adder is _____.

A. 3

B. 1

C. 2

D. 4

Q.2 In 8x1 multiplexer, which one of the following lines must always be connected to ground in order to activate the mutiplexer?

A. G'

B. W

C. Vcc

D. Y

Q.3 A counter circuit is usually constructed of _____

A. A number of NAND gates connected in cascade form

B. A number of NOR gates connected in cascade form

C. A number of flip-flops connected in cascade

D. A number of latches connected in cascade form

Q.4 Three decade counter would have _____

A. 5 BCD counters

B. 4 BCD counters

C. 2 BCD counters

D. 3 BCD counters

Q.5 How many select lines would be required for an 8x1 multiplexer?

A. 8

B. 3

C. 1

D. 2
