CS302P - Quiz No.9

Date: 11 July 2025

Q.1 Ripple counters are also called _____

A. Asynchronous counters

B. Synchronous counters

C. SSI counters

D. VLSI counters

Q.2 Following diagram is of _____ code conversion.
https://storage.googleapis.com/tb-img/production/20/09/F1_S.B_Deepak_03.03.2020_D%201.png

A. Gray

B. BCD

C. Excess-3

D. ASCII

Q.3 In a comparator, if we get input as A>B then the output will be _____

A. A

B. 0

C. B

D. 1

Q.4 To create a Johnson Counter by using D-flip flops, how flip flops should be connected together?

A. Q output of previous flip flop should be connected to D input of second flip flop

B. Q' output of previous flip flop should be connected to D input of second flip flop

C. Q output of previous flip flop should be connected to clock input of second flip flop

D. Q' output of previous flip flop should be connected to clock input of second flip flop

---

Q.5 Which one is a basic comparator?

A. OR

B. NAND

C. XOR

D. AND
