Q.1 NAND gate is form by connecting _____

A. OR Gate and then AND Gate
B. NOT Gate and then AND Gate
C. AND Gate and then OR Gate
D. AND Gate and then NOT Gate

Q.2 Digital Systems are based on the _____ system.

A. Decimal Number
B. Hexadecimal Number
C. Caveman Number
D. Binary Number

Q.3 The maximum decimal number that can be represented using the 64-bit unsigned representation is _____.

A. 2^63
B. 2^64
C. (2^64)-1
D. (2^64)+1

Q.4 The measurable values generally change over a _____.

A. Discrete range
B. Continuous range
C. Specific period
D. Time

Q.5 The _____ Gate is used in applications where the output signal is a 1 when any one input is a 1.

A. NOT
B. XOR
C. AND
D. OR

Q.6 _____ is an essential part of sequential circuit.

A. Multiplexers
B. JK Flip Flop
C. Memory Element
D. Clock

VU TOOLKIT

Q.7 The digital circuits operate with which combination of values given below?

A. 0 volts, 0 volts

B. +5 volts, 0 volts

C. -5 volts, +5 volts

D. -5 volts, 0 volts

Q.8 A _____ is converted into a standard POS by using the rule AA^{-}= 0.

A. Simplified POS

B. Non-standard SOP

C. Simplified SOP

D. Non-standard POS

Q.9 In the 32-bit Single Precision Floating Point format, the exponent value _____ is reserved to represent infinity exponents.

A. 99

B. 255

C. 98

D. 256

Q.10 Demorgan's two theorems prove the equivalency of the NAND and _____ gates and the NOR and _____ gates respectively.

A. Positive-OR, Negative-AND

B. Negative-AND, Positive-OR

C. Positive-OR, Positive-AND

D. Negative-OR, Negative-AND

VU TOOLKIT