Q.1 The Binary number 1011.101 has an Integer part represented by ____ and a fraction part ___ separated by a decimal point.

A. 10111, 11

B. 101, 1011

C. 101, 1101

D. 1011, 101

Q.2 _____ Device dissipate varying amount of power depending upon the frequency of operation.

A. CMOS

B. Storage

C. Peripheral

D. TTL

Q.3 Power dissipation of ____ devices remains constant throughout their operation.

A. TTL

B. Peripheral

C. CMOS

D. Storage

Q.4 NOR gate is form by connecting _____

A. AND Gate and then OR Gate

B. NOT Gate and then OR Gate

C. OR Gate and then NOT Gate

D. OR Gate and then AND Gate

Q.5 A.(B + C) = A.B + A.C is the expression of _____

A. Commutative Law

B. Distributive Law

C. Demorgan's Law

D. Associative Law

Q.6 High level Noise Margins (VNH) of CMOS 5 volt series circuits is _____

A. 0.3 V

B. 0.9 V

C. 0.5 V

D. 3.3 V

Q.7 Consider the sum of weight method for converting decimal into binary value, _____ is the highest weight for 411.

A. 64

B. 512

C. 128

D. 256

Q.8 The _____Gate is used in circuits to generate the 1's Complement of a number by inverting all its bits.

A. XOR

B. NOT

C. AND

D. OR

Q.9 A _____ is converted into a standard POS by using the rule AA^{-}= 0.

A. Simplified POS

B. Non-standard POS

C. Simplified SOP

D. Non-standard SOP

Q.10 A SOP expression having a domain of 3 variables will have a truth table having ___ combinations of inputs and corresponding output values.

A. 4

B. 8

C. 2

D. 16

VU TOOLKIT